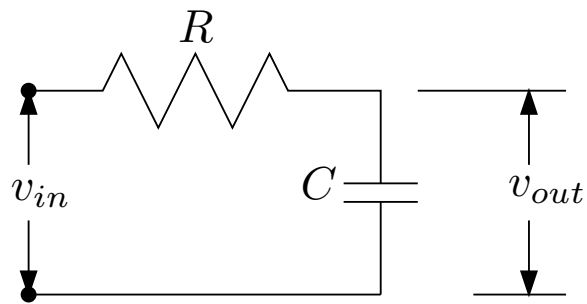


ME 458 Mechatronics
Low-pass Filter Homework



1. Derive the transfer function between v_{out} and v_{in} .
2. What is the corner frequency f_c of this filter if $R=1\text{ k}\Omega$ and $C=10\text{ }\mu\text{F}$? Be sure to answer in Hz.
3. If v_{in} is a sine wave with amplitude 1.0, what is v_{out} at the following frequencies?
 - $0.5 f_c$
 - f_c
 - $10 f_c$

Be sure to include magnitude and phase in your answers.