

1. (4 points) Find the transfer function between v_{out} and v_{in} .

$$v_{in} - iR - L \frac{di}{dt} = 0 \quad (1)$$

$$V_{in} = IR + LsI \quad (2)$$

$$I = \frac{1}{R + Ls} V_{in} \quad (3)$$

$$v_{out} = L \frac{di}{dt} \quad (4)$$

$$V_{out} = LsI \quad (5)$$

Substituting for I from equation 3 gives

$$V_{out} = \frac{1}{R + Ls} Ls V_{in} \quad \text{or} \quad \frac{V_{out}}{V_{in}} = \frac{Ls}{Ls + R} = \frac{s}{s + R/L} \quad (6)$$

If $R = 100 \, \Omega$, $L = 15 \, \text{mH}$ ($15 \times 10^{-3} \, \text{H}$), and $v_{in} = \sin(2\pi ft)$, find the magnitude and phase of v_{out} for $f = 1 \, \text{Hz}$, $100 \, \text{Hz}$, and $10,000 \, \text{Hz}$.


$$TF = \frac{s}{s + p} \quad (7)$$

where $p = R/L = 6666.667 \, \text{rad/sec}$ or $1061 \, \text{Hz}$. Evaluate TF at $s = 2.0j\pi [1 \quad 100 \quad 10000]$:

f (Hz)	Mag.	Phase (deg.)
1	0.0009425	89.95
100	0.09383	84.62
10000	0.9944	6.06


Extra credit (1 point) What is this circuit called? What does it do?

The circuit is a high-pass filter.

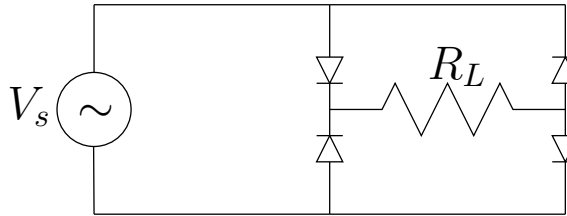


2. (3 points) Assuming ideal diodes, draw equivalent circuits for $V_s > 0$ and $V_s < 0$.


$V_s > 0$:

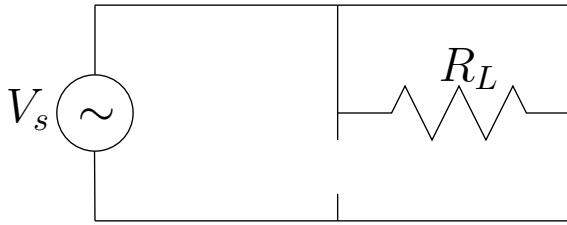


$V_s < 0$:

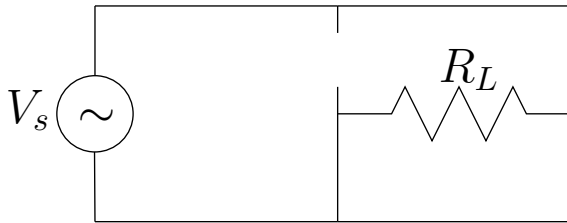


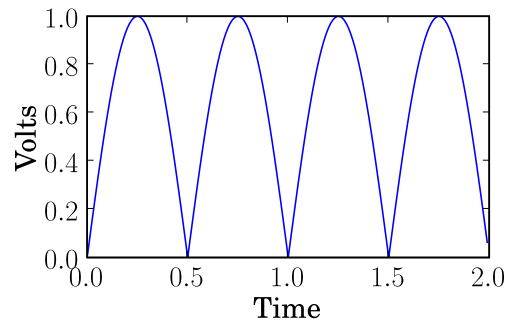If V_s is a sine wave, sketch the voltage across R_L (assuming ideal diodes).




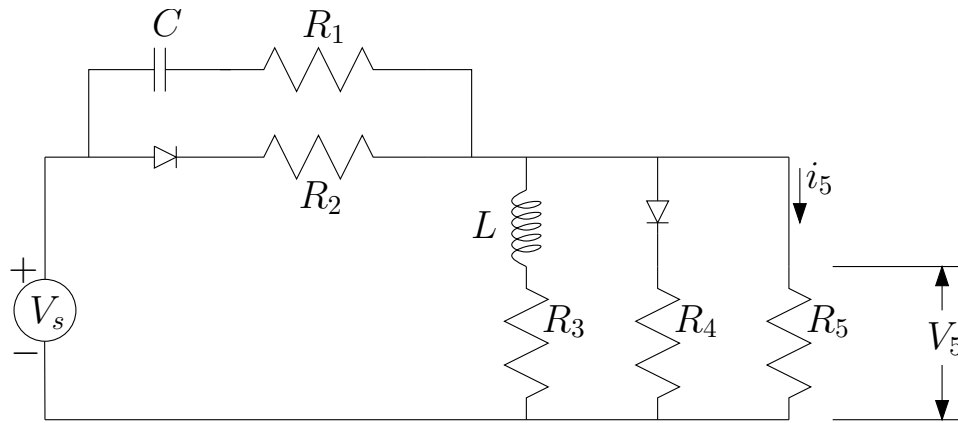

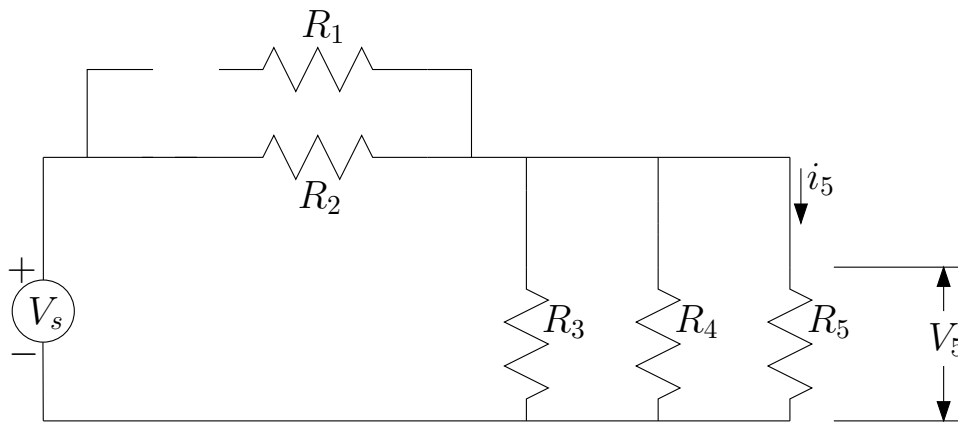3. (3 points) If V_s is a DC voltage, draw the equivalent DC circuit.



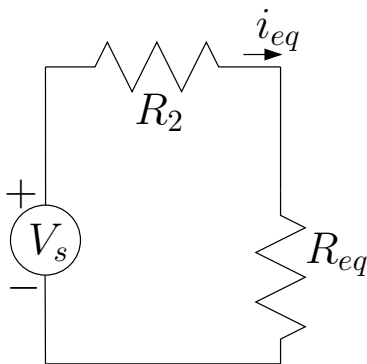If $V_s = 5\text{V DC}$, $R_1 = 1\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, $R_3 = 3\text{ k}\Omega$, $R_4 = 4\text{ k}\Omega$, and $R_5 = 5\text{ k}\Omega$, find V_5 and i_5 .



$$R_{eq} = \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)^{-1} = 1276.6 \Omega \quad (8)$$

$$V_s = R_2 i_{eq} + R_{eq} i_{eq} \quad (9)$$

$$i_{eq} = \frac{V_s}{R_2 + R_{eq}} = 0.001526 \text{ A} \quad (10)$$

$$V_{eq} = V_5 = i_{eq} R_{eq} = 1.948 \text{ V} \quad (11)$$

$$i_5 = \frac{V_5}{R_5} = 0.0003896 \text{ A} \quad (12)$$