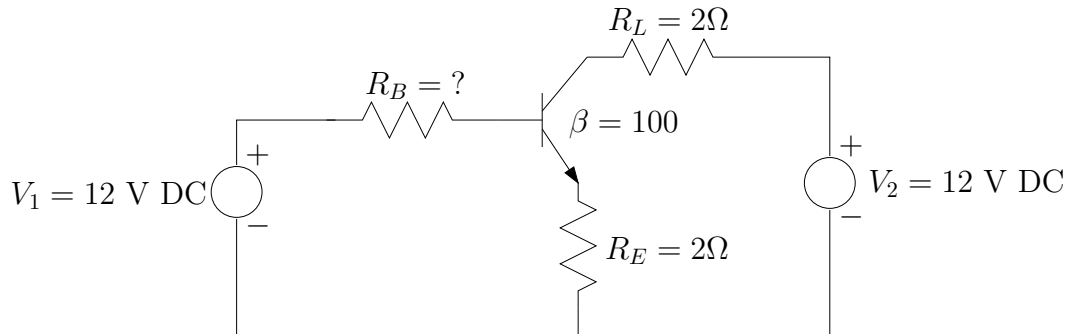


1. (2 points) What does a transistor do? What is an example of a practical use of a transistor in a mechatronic application? What are some indicators that a transistor might be necessary in a certain application?

A transistor is a current controlled switch or a current amplifier. It is used whenever a high current load needs to be controlled by a computer. (Could also be used to control a high voltage load, such as using a 5V DC computer signal to turn 120V AC devices on and off.)



2. (4 points) If the magnification factor for the transistor is  $\beta = 100$ , what resistance  $R_B$  should be used in the above circuit to ensure that the transistor is fully saturated? (Assume the transistor is real NOT ideal).

KVL for right loop:

$$12 - R_L i_c - V_{ce} - R_E i_e = 0 \quad (1)$$

KVL for left loop:

$$12 - R_b i_b - V_{BE} - R_E i_e = 0 \quad (2)$$

$$i_c = \beta i_b \quad (3)$$

$$i_e = i_c + i_b \text{ or } i_e = i_c \left(1 + \frac{1}{\beta}\right) \quad (4)$$

$$V_{ce} = 0.2 \quad (5)$$

$$V_{be} = 0.7 \quad (6)$$

$$\beta = 100 \quad (7)$$


Substituting (4), (5), and (7) into (1) gives

$$11.8 = R_L i_c + R_E 1.01 i_c \quad (8)$$

or  $i_c = 2.935$  A. Knowing  $i_c$  gives  $i_e = 2.9647$  A and  $i_b = 0.02935$  A. Plugging  $i_e$  and  $i_b$  into (2) gives

$$0.02935 R_b = 5.3706 \quad (9)$$

or  $R_b = 182\Omega$ .

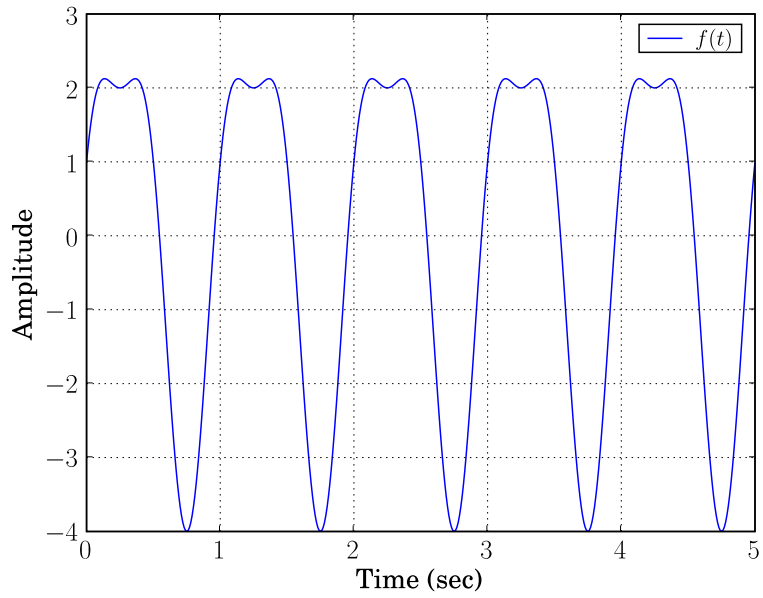

3. (4 points) In the above graph,  $f(t) = 3.0 \sin(2\pi t) + \cos(4\pi t)$ . What is the fundamental frequency  $\omega_0$ ? What are the Fourier coefficients  $a_1$ ,  $b_1$ ,  $a_2$ , and  $b_2$ ?

$$\omega_0 = 2\pi \text{ rad/sec of } 1 \text{ Hz}$$

$$\begin{aligned} a_1 &= 0 \\ b_1 &= 3 \\ a_2 &= 1 \\ b_2 &= 0 \end{aligned}$$