

ECE 476 - Spring 2021
Chapter 7 Problems

January 7, 2021

Problem 1. Common-Emitter (CE) Amplifier

Textbook problem: 7.125 (Hint: What author calls R_{in} , I call R'_{in} .)

Problem 2. Common-Emitter (CE) Amplifier

Textbook problem: 7.129

Problem 3. CE Amplifier With Emitter Degeneration

Textbook problem: 7.58

Assume $\beta = 250$ and determine the following:

- The input resistance looking directly into the base of the BJT, R_{in} .
- The input resistance as seen by the source, R'_{in} .
- The voltage gain, $A_v = \frac{v_{o2}}{v_i}$.

There is no need to derive the voltage gain expressions since we did that in class.

Problem 4. Emitter Follower

Textbook problem: 7.134 (Just assume $\beta = 125$.)