
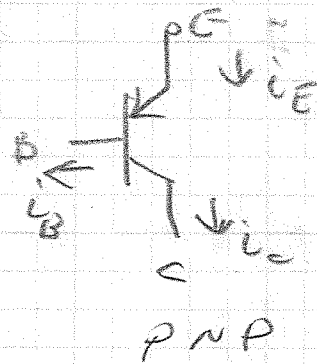


LECTURE # 1

Review

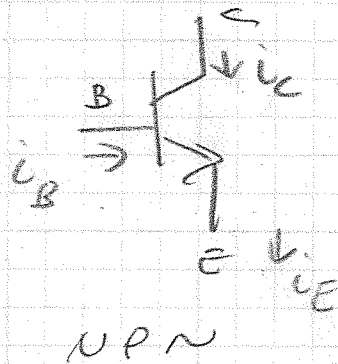

$$I_E = I_B + I_C$$

ALWAYS


$$I_C = \beta I_B$$

of ACTIVE — BE forward bias
BC reverse bias


$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_C = \alpha I_E$$

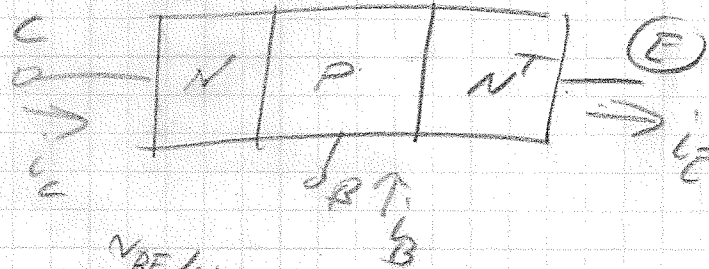

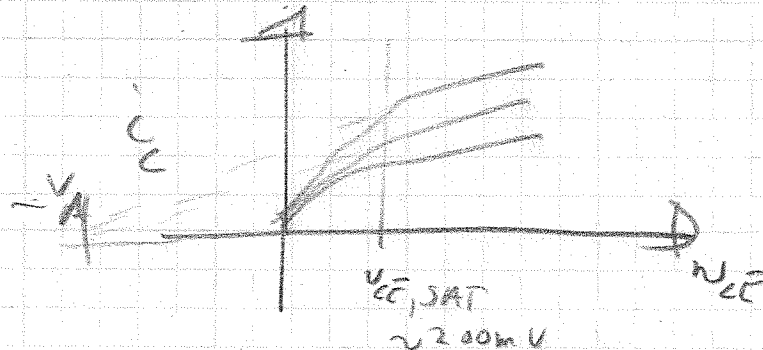
$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CE}}{V_A} \right)$$




Small-signal hybrid- π model

(2)

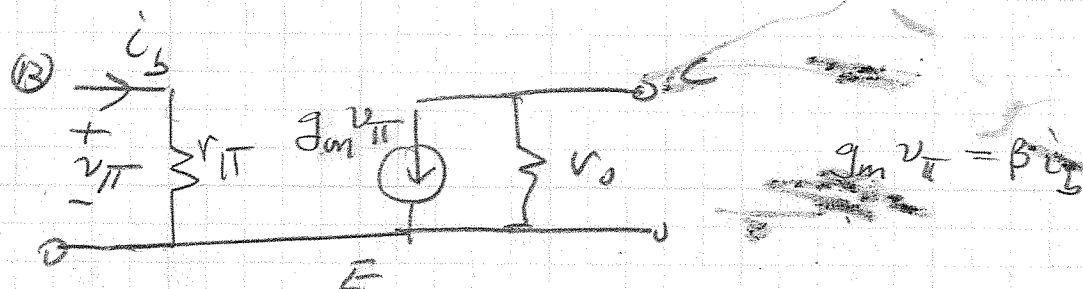

$$g_m = \frac{I_C}{V_T}, \quad r_{\pi} = \frac{\beta}{g_m}, \quad r_o = \frac{V_A}{I_C}$$


Amplifier topologies

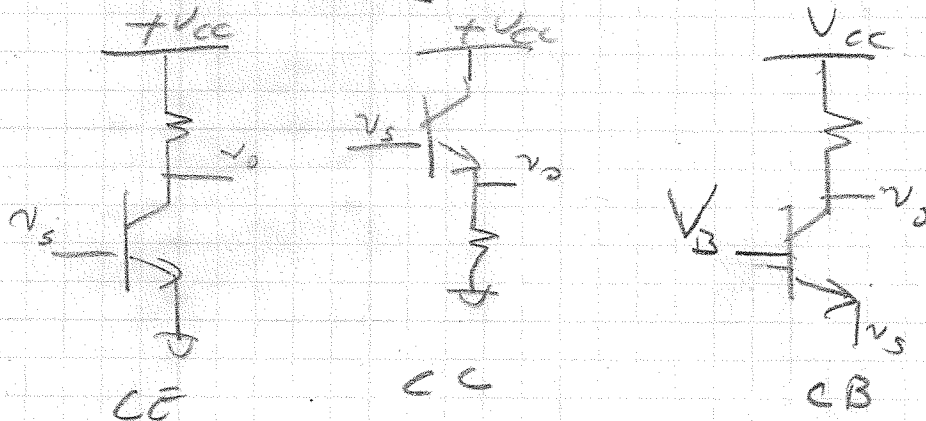

Start with CE ampl. prer

3

See (Sect 7.5.2) page 470

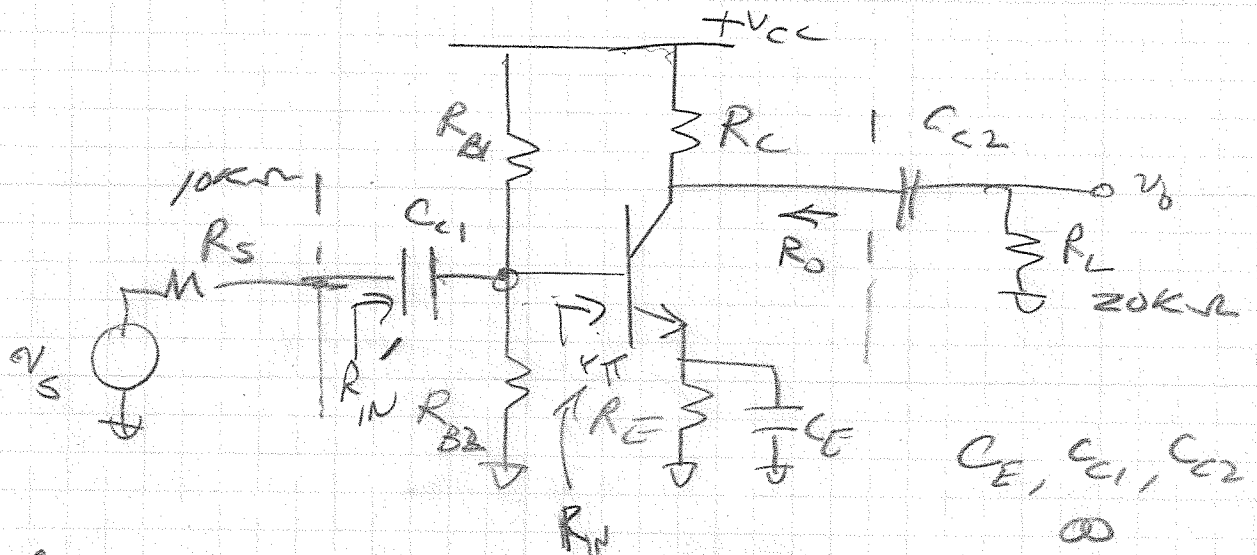

Let's do exercise on p 471

Want $I_E = 0.5 \text{ mA}$, $V_C = 6 \text{ V}$.

Want current through R_{B2} of $50 \mu\text{A}$ & $V_B = 5 \text{ V}$

Assume $V_{CE} = 15 \text{ V}$, $\beta = 100$, $V_{BE} = 0.7 \text{ V}$, $V_A = 100 \text{ V}$

Find R_C , R_E , R_{B1} , R_{B2} & A_v

Solve DC problem first!

$$I_C = \left(\frac{\beta}{\beta+1}\right) I_E = \left(\frac{100}{101}\right) (0.5 \text{ mA}) = 495 \mu\text{A}$$

$$\text{If } V_C = 6 \text{ V then } R_C = \frac{V_{CC} - V_C}{I_C} = \frac{15 - 6}{0.495 \text{ mA}}$$

$$R_C = 18.2 \text{ k} \sim \boxed{18 \text{ k}\Omega} \leftarrow R_C$$

$$\text{If } I_E = 0.5 \text{ mA then } I_B = \frac{500 \mu\text{A}}{101} = 9.95 \mu\text{A}$$

$$\text{If } V_B = 5 \text{ V & } I_{B2} = 50 \mu\text{A, then}$$

$$R_{B2} = \frac{5 \text{ V}}{50 \mu\text{A}} = \boxed{100 \text{ k}\Omega} \leftarrow R_{B2}$$

Can also easily find R_E

④

$$V_E = V_B - V_{BE(on)} = 5V - 0.7V = 4.3V$$


$$R_E = \frac{V_E}{I_E} = \frac{4.3V}{0.5mA} = \boxed{8.6K\Omega} \leftarrow R_E \checkmark$$

Still need to find R_{B1} !

$$I_{B1} = I_{B2} + I_B = 50\mu A + 4.95\mu A$$

$$R_{B1} = \frac{15 - 5V}{54.95\mu A} = \boxed{182K\Omega} \leftarrow R_{B1} \checkmark$$

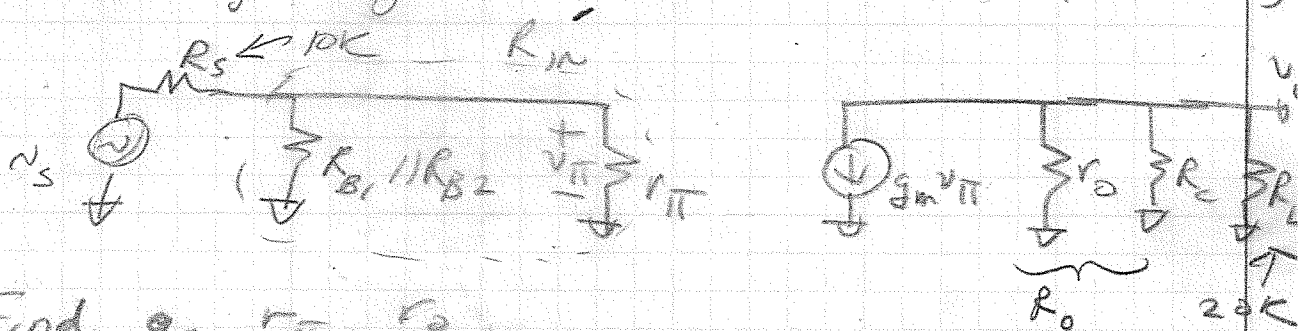Small-signal equivalent. (Assume $R_S = 10K$, $R_L = 20K$)



Find g_m , r_{π} , r_o

$$g_m = \frac{I_C}{V_T} = \frac{495\mu A}{25.9mV} = 19.1mS \quad \left(\begin{array}{l} I_{C \text{ use}} \\ V_T = 25.9mV \end{array} \right)$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{19.1mS} \approx 5.2K\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100V}{0.495mA} = 202K\Omega$$

$$R'_{IN} = R_{B1} \parallel R_{B2} \parallel r_{\pi} = 4.8K\Omega \approx r_{\pi}$$

$$R_o = r_o \parallel R_C = 16.5K\Omega$$

$$R_{IN} = r_{\pi}$$

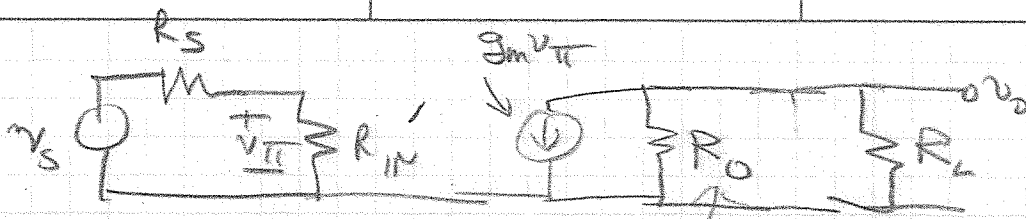

$$v_o = -g_m (R_0 \parallel R_L) \left[\frac{R_{in}}{R_s + R_{in}} \right]$$

$\uparrow$ 14.5K $\uparrow$ 20K $\uparrow$ 10K $\nwarrow$ 4.8K $\swarrow$ 4.8K


$$\frac{A_v}{v_o} =$$

$$\frac{v_o}{v_s} = - (172.7) (0.324) = -55.9 \frac{V}{V}$$

$$\frac{v_o}{v_i} = -g_m (R_0 \parallel R_L)$$

$\sim 35\text{dB}$
of gain!


Let's try another one.

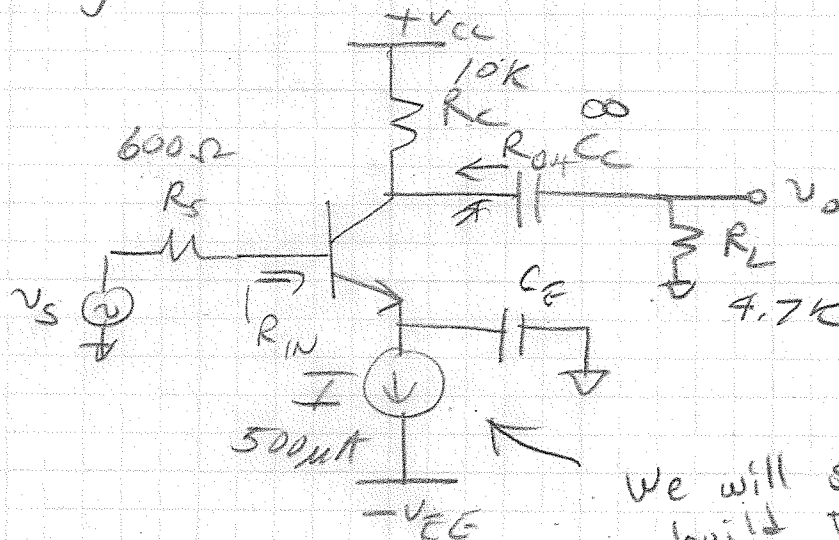

We will see how to build this in later chapter.

Assume $\beta = 150$, $V_A = 125V$

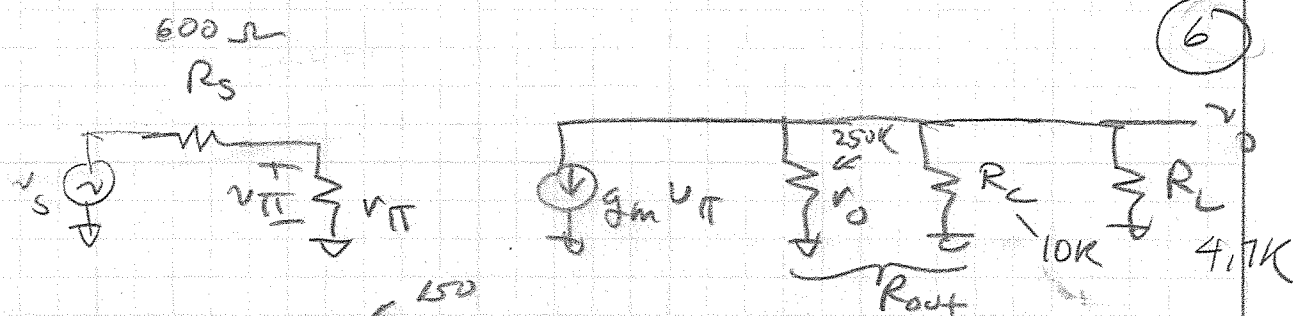Find $A_v = \frac{v_o}{v_s}$, R_{in} , R_{out}



$$g_m = \frac{I_C}{U_T} = \frac{(150)(\beta+1)(I_E)}{U_T} \approx \frac{I_E}{U_T} = \frac{0.5 \text{ mA}}{25.9 \text{ mV}}$$

$$g_m = 19.3 \text{ mS}$$

$$r_{\pi} = R_{IN} = \frac{\beta}{g_m} = \frac{150}{19.3 \text{ mS}} \approx 7.8 \text{ K}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{V_A}{I_E} = \frac{125 \text{ V}}{0.5 \text{ mA}} = 250 \text{ K}\Omega$$


$$R_o = r_o \parallel R_C \approx 9.6 \text{ K}\Omega$$

$$\begin{aligned} A_v &= - \left[\frac{R_{IN}}{R_{IN} + R_s} \right] [g_m (R_o \parallel R_L)] \\ &= - \left[\frac{7.8 \text{ K}\Omega}{7.8 \text{ K}\Omega + 0.6 \text{ K}\Omega} \right] [19.3 \text{ mS} (3.2 \text{ K}\Omega)] \\ &\approx - (0.9286) (61.8) = -57.4 \\ &\quad \sim 35 \text{ dB} \end{aligned}$$

LECTURE #2

7.5.3

CE amp with Emitter Degeneration.

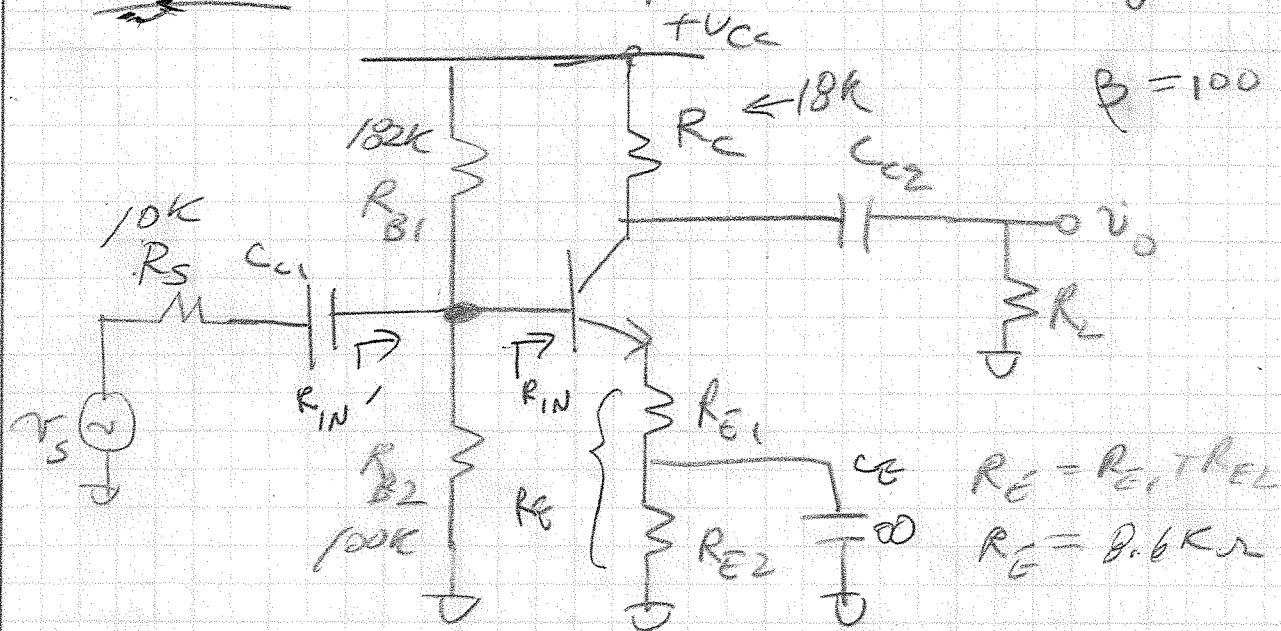

Note we have replaced R_E with two resistors R_{E1} & R_{E2} where $R_E = R_{E1} || R_{E2}$.
 We do this to


- 1) Desensitize the gain, A_v .
 (Make it mostly dependent on R_C/R_{E1})
- 2) Increase the input impedance (w/o β loss)
 It was r_{π} & now its $r_{\pi} + (\beta+1)R_E$

Cost we incur is lower A_v than if we had used a "strict" CE amp.


Exercise 7.4.2 ask that we raise R_{IN}' to 10 K and re-calculate A_v .
If $R_E = R_{E1} + R_{E2}$ then DC solution is the same.

(2)

Small-signal analysis.

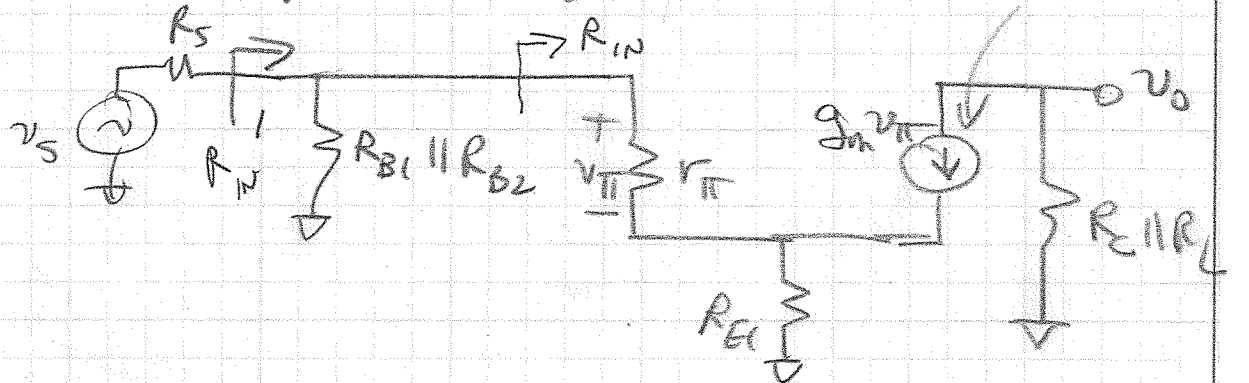

Find R_{IN} then $R_{IN}' = R_{B1} || R_{B2} || R_{IN}$

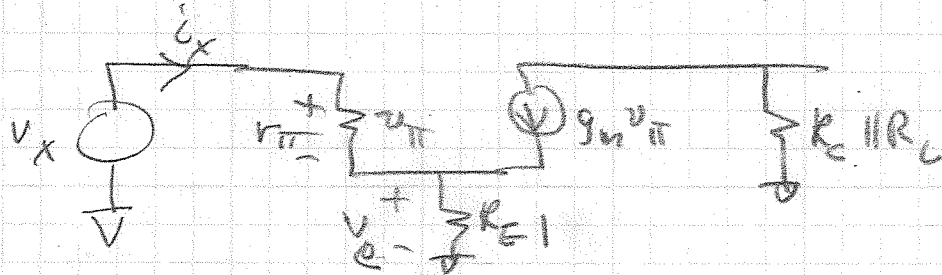

$R_{IN} \equiv \frac{v_x}{i_x}$ = input resistance of a CE amp with emitter deg.

$$v_x = v_e + v_{\pi} \quad \text{where } v_{\pi} = i_x r_{\pi}$$

$$v_x = v_e + i_x r_{\pi}$$

But $v_e = (i_x + g_m v_{\pi}) R_{E1}$ ← KCL

$$\text{So } v_x = [i_x R_{E1} + g_m R_{E1} (i_x r_{\pi})] + i_x r_{\pi}$$

$$v_x \equiv i_x R_{E1} + \beta R_{E1} i_x + i_x r_{\pi}$$

$$R_{in} \equiv \frac{v_x}{i_x} = r_{\pi} + (\beta + 1)R_{E1}$$

*

(3)

Very important

Want $G_{in}' = \frac{1}{R_{in}'} = \frac{1}{10k} = G_{B1} + G_{B2} + G_{in}'$

$$G_{in}' = 100\mu S - \frac{1}{100k} - \frac{1}{182k} = 84.5\mu S$$


So $R_{in}' = 11.8k\Omega$ but $r_{\pi} = 5.2k\Omega$
and $\beta = 100$

$$R_{E1} = \frac{11.8k - 5.2k}{(\beta + 1)} = \boxed{65\Omega}$$

So $R_{E2} = R_E - R_{E1} = 8.2k - 65\Omega \approx \boxed{8.14k\Omega}$

Let's find the voltage gain of a CE amp with emitter degeneration.

Neglect r_o

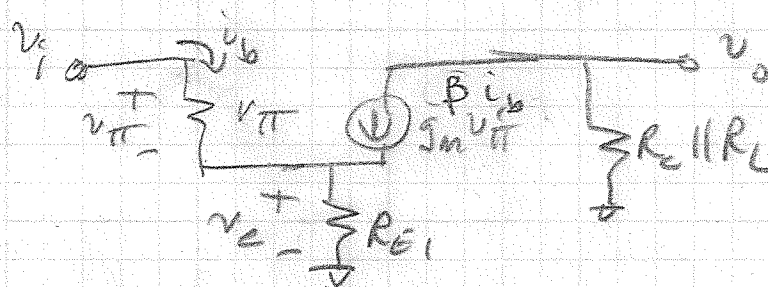

$$R_{out} \approx R_C$$

Find v_o/v_i .

$$v_o = -(g_m v_{\pi})(R_C \parallel R_L)$$

But $v_i = v_{\pi} + v_e \Rightarrow v_{\pi} = v_i - v_e$ (KVL)

where $v_e = (\beta + 1)i_b R_{E1}$ & $i_b = \frac{v_{\pi}}{r_{\pi}} = g_{\pi} v_{\pi}$

$$\Rightarrow v_{\pi} = v_i - (\beta + 1)g_{\pi} R_{E1} v_{\pi}$$

Thus $v_{\pi} = \frac{v_i}{1 + (\beta + 1) g_{\pi} R_{E1}}$

(4)

So we conclude

$$v_o = -g_m (R_C \parallel R_L) v_{\pi}$$

$$\frac{v_o}{v_i} = \frac{-g_m (R_C \parallel R_L)}{1 + (\beta + 1) g_{\pi} R_{E1}}$$

But $\beta + 1 \approx \beta$ and $\beta g_{\pi} = g_m$!

So $\left[\frac{v_o}{v_i} \approx \frac{-g_m (R_C \parallel R_L)}{1 + g_m R_{E1}} \right]^* \text{Important!}$

So gain $1 + g_m R_{E1}$ times smaller than what he had for CE amp!

Also note if $g_m R_{E1} \gg 1 \Rightarrow R_{E1} \gg \frac{1}{g_m}$

then $\frac{v_o}{v_i} \approx \frac{-(R_C \parallel R_L)}{R_{E1}}$ and the gain

is just the ratio of resistor values!

(THIS IS OFTEN VERY DESIRABLE!)

For the entire circuit we get $18K$ $20K$

$$\frac{v_o}{v_s} = \left[\frac{R'_{in}}{R'_{in} + R_s} \right] \left[\frac{-g_m (R_C \parallel R_L)}{1 + g_m R_{E1}} \right]$$

$$g_m = 19.1 \text{ mS}$$

$$g_m R_{E1} = 1.24$$

$\frac{1}{2}$ Since $R_{in} = R_s = 10K$

5


$$\frac{v_o}{v_s} = \underbrace{-\frac{1}{2}}_{\text{was } 0.324} \left(\underbrace{\frac{180.9}{1+1.24}}_{80.8 \leftarrow \text{was } 172.7} \right) = -40.4 \quad \leftarrow 32\text{dB}$$

With CE amp had 35 dB, Now we have 32dB,

7.5.5 CC Amplifier (Emitter Follower)

Voltage gain ~ 1 but we get current and hence power gain! we use this as a buffer!

Do exercise 7.44 (page 477)

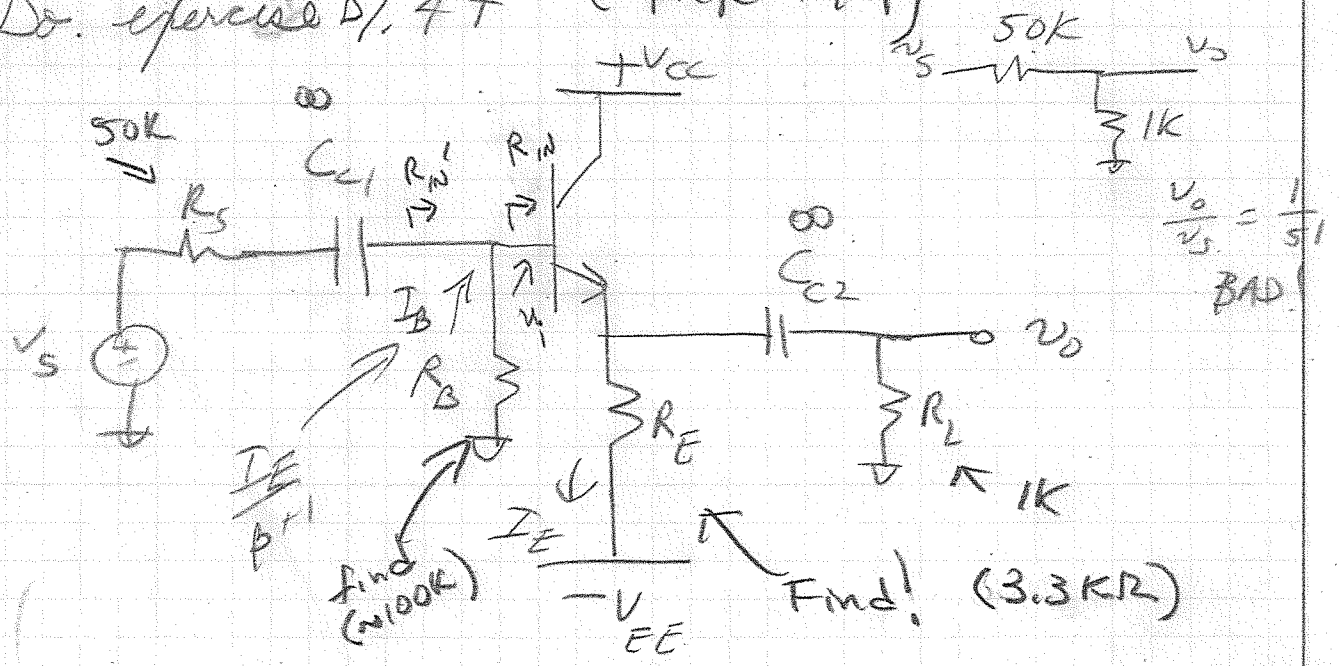

want $I_E = 1\text{mA}$. Allow a DC voltage drop across R_B of 1V. The available power supplies are $\pm 5\text{V}$, $\beta = 100$, $V_{BE(on)} = 0.7\text{V}$ and $V_A = 100\text{V}$.

Also $R_S = 50\text{k}$ & $R_L = 1\text{k}$

Specify values for R_B & R_E !

(6)

$$\text{So } V_B = -1V \Rightarrow V_E = -1V - 0.7 = -1.7V$$

$$\text{Hence } I_E = \frac{-1.7 - (-5)}{R_E} \Rightarrow R_E = \frac{3.3V}{1mA} = 3.3k\Omega$$


$\Rightarrow$ want 1mA

$$R_B = \frac{0 - V_B}{I_B} = \frac{-(\beta+1)(V_E)}{I_E} = \frac{-(101)(-1)}{1mA}$$

$I_B \approx I_E / (\beta+1)$

$$R_B = 101k \approx 100k\Omega$$

Small-signal equivalent

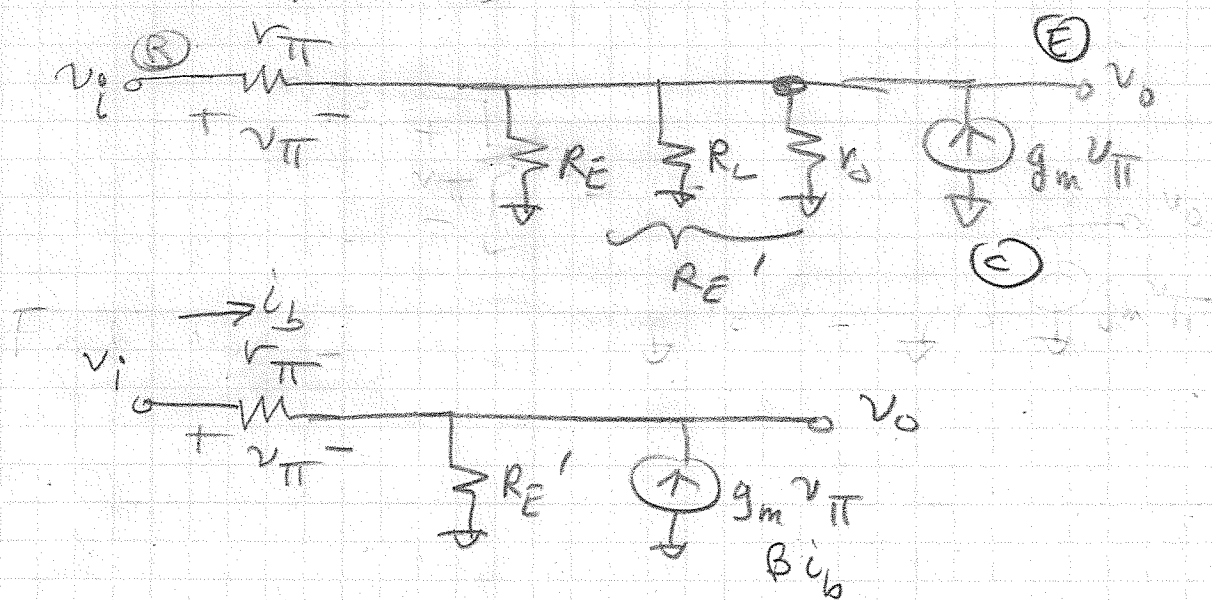

Find $\frac{v_o}{v_i}$

$$v_o = (\beta+1) i_b R_E' \quad \text{but } i_b = g_{\pi} v_{\pi}$$

$$v_o = (\beta+1) g_{\pi} R_E' v_{\pi} = i_e R_E' \quad \leftarrow \beta+1 i_b \leftarrow s_{\pi} v_{\pi}$$

$$\text{But } v_i - v_{\pi} = v_o \Rightarrow v_{\pi} = v_i - v_o$$

$$\text{Hence } v_o = (\beta + 1) g_{\pi} R_E' (v_i - v_o) \quad (7)$$

$$\frac{v_o}{v_i} = \frac{(\beta + 1) g_{\pi} R_E'}{1 + (\beta + 1) g_{\pi} R_E'} \approx \frac{g_m R_E'}{1 + g_m R_E'}$$

$$\boxed{\frac{v_o}{v_i} \approx \frac{g_m R_E'}{1 + g_m R_E'}} \quad * \text{ Important}$$

Can also easily show that

$$R_{in} = r_{\pi} + (\beta + 1) R_E'$$

$$\text{and that } R_{out} = r_o \parallel R_E \parallel \left[\frac{r_{\pi} + R_{Th} \parallel R_B}{\beta + 1} \right]$$

$$g_m = \frac{I_C}{V_T} \approx \frac{I_E}{V_T} \leftarrow 1 \text{ mA} \quad \text{since } I_E = \left(\frac{\beta + 1}{\beta} \right) I_C$$

$$g_m = \frac{1 \text{ mA}}{25.9 \text{ mV}} \approx 38.6 \text{ mS}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{38.6 \text{ mS}} \approx 2.6 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} \approx \frac{V_A}{I_E} = \frac{100 \text{ V}}{1 \text{ mA}} = 100 \text{ k}\Omega$$

$$R_E' = R_E \parallel r_o \parallel R_L \approx 0.76 \text{ k}\Omega$$

$\uparrow \quad \quad \uparrow \quad \quad \uparrow$
 $3.3 \text{ k}\Omega \quad 100 \text{ k}\Omega \quad 1 \text{ k}\Omega$

$$R_{in} = 2.6 \text{ k}\Omega + (101)(0.76 \text{ k}\Omega) \approx 79 \text{ k}\Omega$$

$$R_{in}' = R_{in} \parallel R_B \approx 44.1 \text{ k}\Omega$$

$\uparrow \quad \quad \uparrow$
 $79 \text{ k}\Omega \quad 100 \text{ k}\Omega$

8

$$\frac{v_o}{v_s} = \left(\frac{v_i}{v_s} \right) \left(\frac{v_o}{v_i} \right)$$

$$\frac{v_o}{v_s} = \left(\frac{R_{IN}'}{R_{IN}' + R_s} \right) \left(\frac{g_m R_E'}{1 + g_m R_E'} \right)$$

$$= \left[\frac{44.1 \text{ k}\Omega}{44.1 \text{ k}\Omega + 50 \text{ k}\Omega} \right] \left[\frac{(38.6 \text{ mV})(0.76 \text{ k}\Omega)}{1 + (38.6 \text{ mV})(0.76 \text{ k}\Omega)} \right]$$

29.3

← -7.1 dB

$$\approx (0.47) (0.967) = 0.454$$


$$R_{out} = 100 \text{ k}\Omega \parallel 3.3 \text{ k}\Omega \parallel \left[\frac{\frac{2.6 \text{ k}\Omega}{r_{\pi} + (R_B \parallel R_s)}}{\beta + 1} \right] \parallel 33 \text{ k}\Omega$$

352 Ω

≈ 317 Ω
≈ 320 Ω

①


Analyze the following CE amp.

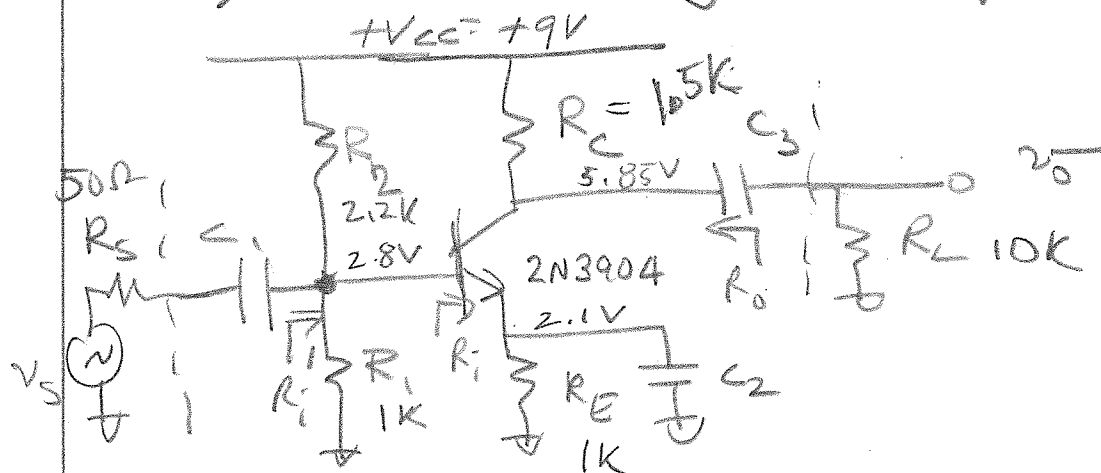


Assume $C_1, C_2, C_3 \rightarrow \infty$, $V_{BE(ON)} = 0.7$
 $\beta = 150$
 $V_A = 75V$

Find I_C , $A_V = \frac{V_o}{V_s}$, R_i , R_i' , R_o

Solve DC problem first.

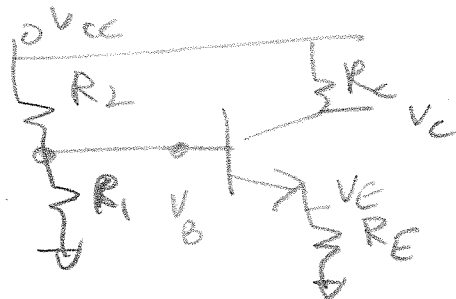

"Thevenize"

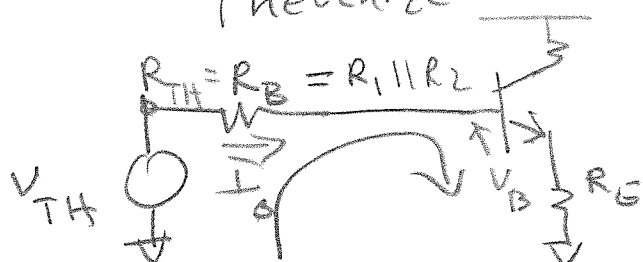

$$R_B = R_1 \parallel R_2 \approx 688\Omega$$

$$V_{TH} = \left(\frac{R_1}{R_1 + R_2} \right) V_{CC}$$

$$V_{TH} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$\boxed{I_B = \frac{V_{TH} - V_{BE}}{R_B + (\beta + 1)R_E}} \quad *$$

(2)

In well designed amplifier we like

$V_{TH} \sim \frac{1}{3} V_{CC}$, I_C a few mA.

$$R_B \gg R_S$$

$$R_B \ll (\beta + 1)R_E \quad \text{why?}$$

$$\text{If } (\beta + 1)R_E \gg R_B$$

$$I_B = \frac{V_{TH} - V_{BE}}{(\beta + 1)R_E} \Rightarrow I_C = \frac{\beta}{\beta + 1} \left(\frac{V_{TH} - V_{BE}}{R_E} \right)$$

$$* \boxed{I_C \approx \frac{V_{TH} - V_{BE}}{R_E}} \quad \text{if } \beta \gg 1$$

Note here

$$V_{TH} = \left(\frac{R_1}{R_1 + R_2} \right) V_{CC} = \left(\frac{1K}{3.2K} \right) (9V) \approx 2.8V$$

$$V_B = V_{TH} - I_B R_B = V_{TH} - \left(\frac{R_B}{(\beta + 1)R_E} \right) (V_{TH} - V_{BE})$$

$$V_B \approx V_{TH} \quad \text{Note here } \frac{R_B}{(\beta + 1)R_E} = \frac{(1K)(2.2K)}{(151)(1K)} = 4.55 \times 10^{-3} \checkmark$$

$$V_E = V_B - V_{BE} \approx V_{TH} - V_{BE} \\ \approx 2.8V - 0.7V = 2.1V$$

$$I_E = \frac{2.1V}{1K} = 2.1mA \sim I_C \quad (I_C = \frac{\beta}{\beta + 1} I_E)$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{2.1mA}{151} \approx 14\mu A$$

$$V_C = V_{CC} - I_C R_C$$

$$V_C = 9V - (2.1 \mu A)(1.5K)$$

$$V_C = 5.85V$$

(3)

Now compute small-signal parameters

$$g_m = \frac{I_C}{V_T} = \frac{2.1 \mu A}{25.9 mV} = 81.1 \mu S$$

$$r_o = \frac{V_A}{I_C} = \frac{75V}{2.1 \mu A} = 35.7 K\Omega$$

$$r_{\pi} = \beta / g_m = \frac{150}{81.1 \mu S} = 1.85 K\Omega$$

$$A_V = \frac{v_o}{v_s} = \frac{v_b}{v_s} \cdot \frac{v_o}{v_b}$$

Find $\frac{v_b}{v_s}$




$$R_i' = R_B \parallel R_i$$

$\uparrow$
 688Ω

$$r_{\pi} = 1.85 K\Omega$$


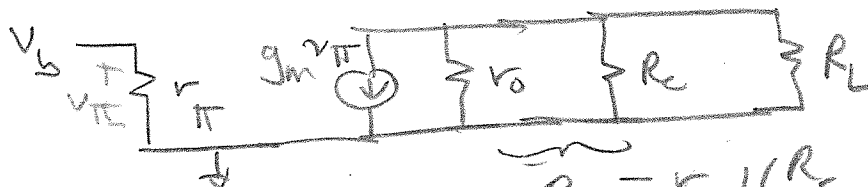
$$\frac{v_b}{v_s} = \frac{501}{551} = 0.909 \leftarrow -0.8 dB$$



$$v_{\pi} = v_b$$

$$R_o = r_o \parallel R_C \approx 1.4 K$$

$$R_L' = R_L \parallel R_o \approx 1.25 K$$

4

$$\begin{aligned}\frac{v_o}{v_b} &= -g_m R_L' = A \\ &= -(81.1 \text{ mS})(1.25 \text{ k}) \\ &\approx -102 \quad \sim 40 \text{ dB}\end{aligned}$$


$$\begin{aligned}A_v = \frac{v_o}{v_s} &= (0.909)(102) = -92.9 \\ &\sim 39.4 \text{ dB}\end{aligned}$$

$$\begin{aligned}R_o &= R_c \parallel r_o \\ R_i &= r_{\pi} \\ R_i' &= r_{\pi} \parallel R_B \\ A &= -g_m R_L' \\ A_v &= \left[\frac{R_i'}{R_i' + R_s} \right] A\end{aligned}$$

cheat sheet

①

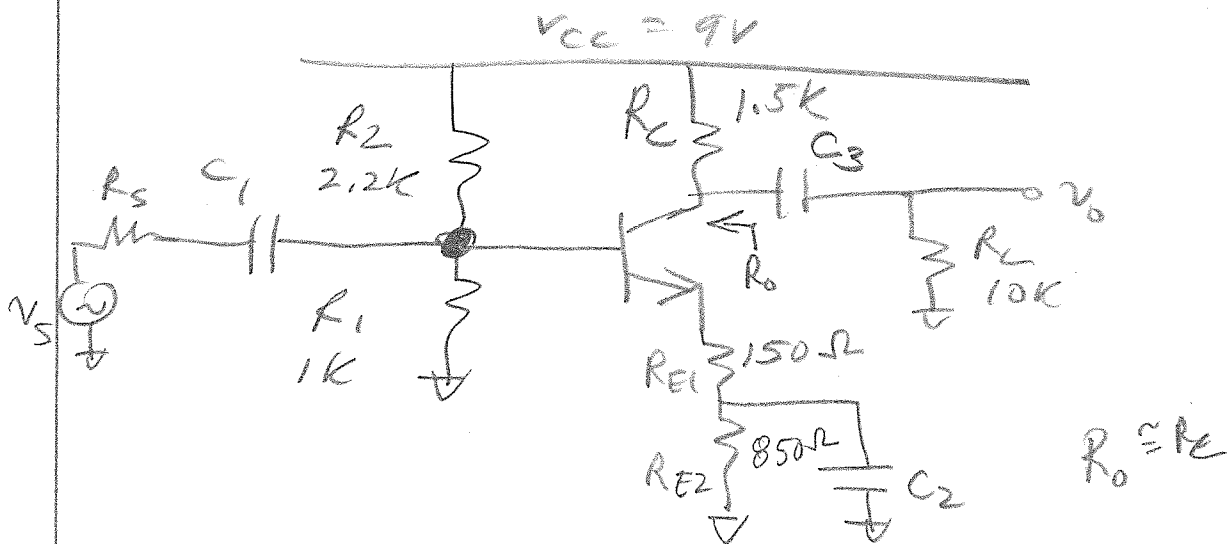Analyze the following CE amp with emitter degeneration circuit



Note $R_{E1} + R_{E2} = R_E = 1K$

DC conditions same as in previous problem.

$$I_C = 2.1 \text{ mA}$$

$$g_m = 81.1 \text{ mS}$$

$$r_o = 35.7 \text{ k}\Omega$$

$$r_{\pi} = 1.85 \text{ k}\Omega$$

$$R_i' = R_B \parallel [r_{\pi} + (\beta + 1)R_{E1}] = 669 \Omega$$

$\underbrace{24.5 \text{ k}\Omega}_{R_B} \parallel \left[\underbrace{1.85 \text{ k}\Omega}_{r_{\pi}} + (\beta + 1) \underbrace{150 \Omega}_{R_{E1}} \right]$
 $\underbrace{688 \Omega}_{R_B} \parallel \underbrace{1.85 \text{ k}\Omega}_{r_{\pi}} \parallel \underbrace{150 \Omega}_{R_{E1}}$

$$\frac{V_b}{V_s} = \frac{669}{669 + 50} = 0.93$$

$$\frac{v_o}{v_b} = -\frac{g_m R_L'}{1 + g_m R_{E1}} = -\frac{g_m (R_C \parallel R_L)}{1 + \underbrace{(81.1 \text{ mV})(150)}_{12.2}}$$

$$= -\frac{(81.1 \text{ mV})(10 \text{ k} \parallel 1.5 \text{ k})}{13.2}$$



$$= -\frac{105.8}{13.2} \approx -8 \quad \text{Note } \frac{1.5 \text{ k}}{150} = 10$$

$$-\frac{g_m R_L'}{1 + g_m R_{E1}} \approx -\frac{R_L'}{R_{E1}} \approx -10$$

If supply voltage changes there will be a much smaller percentage change in the gain of the circuit.

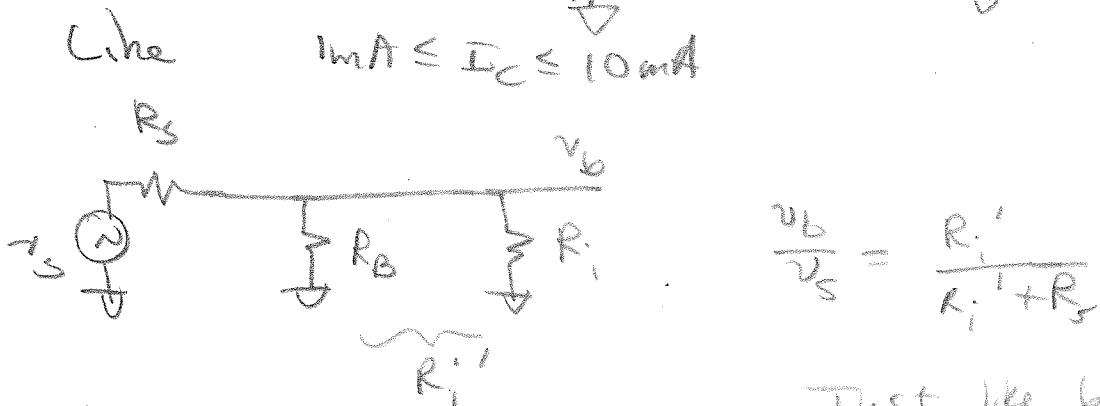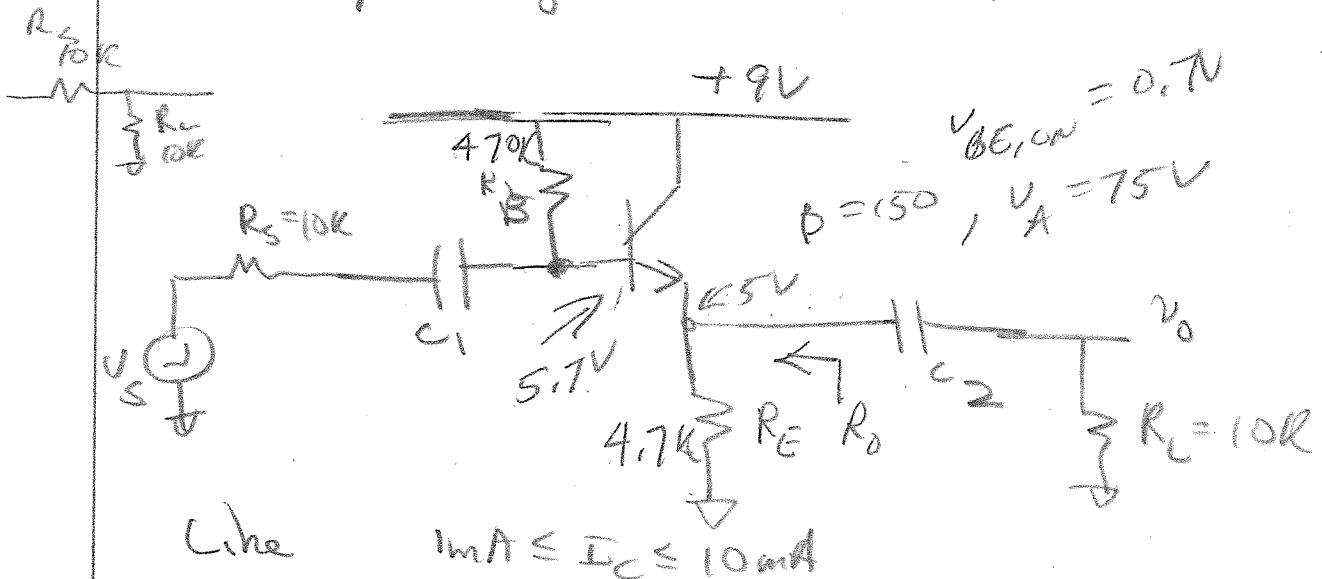7.5.5 CC Amplifier (A.K.A Emitter Follower)

Voltage gain ≈ 1 but we set current and hence power gain. We use this as a buffer



Just like before

$$R_i' = R_i \parallel R_b \quad R_i = r_{\pi} + (\beta + 1) R_i'$$

$$R_E' = R_E \parallel r_o \parallel R_L$$

$$A_v = \left[\frac{R_i'}{R_i' + R_s} \right] \left[\frac{g_m R_E'}{1 + g_m R_E'} \right] = \frac{v_o}{v_s}$$

$$\frac{I}{B} = \frac{V_{CC} - V_{BE(\text{or})}}{R_B + (\beta + 1)R_E} = \frac{9 - 0.7}{970k + (151)(4.7k)}$$

$$R_o = R_E \parallel r_o \parallel \left[\frac{r_{\pi} + R_E'}{B+1} \right] \quad \begin{matrix} R_S \parallel R_B \\ \sim R_S \end{matrix} \quad (3)$$

$$R_o = 4.7k \parallel 20.8k \parallel \left[\frac{3.7k + 10k}{151} \right]$$

$$\boxed{R_o \approx 91\Omega}$$

$$\sim 91\Omega$$

Note if $R_L = 1k$ then

$$A = \frac{g_m R_E'}{1 + g_m R_E'} \approx \frac{(40.9mV)(1k)}{1 + (40.9mV)(1k)}$$

$$A \approx 0.976$$

$$R_i' = r_{\pi} + (B+1)R_E'$$

$$R_i' \approx 3.7k + (151)(1k)$$

$$R_i' \approx 154.7k$$

$$A_v \approx \left[\frac{154.7k}{154.7k + 10k} \right] (0.976)$$

$$\approx 0.92 \quad (-0.7dB)$$

Still quite good