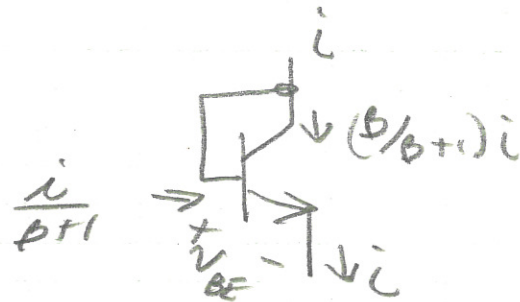


# Chapter 8 Notes ECE 476 Sp16 1

## Diode-connected BJT



$$\underbrace{\frac{i}{\beta+1}}_{i_B} + \underbrace{\left(\frac{\beta}{\beta+1}\right)i}_{i_C} = \underbrace{\left(\frac{\beta+1}{\beta+1}\right)i}_{i_E} = i$$

F.B = forward bias


Acts just like normal BJT. It's the way diodes are implemented on a IC

$$i = i_E = I_{ES} \left( e^{v_{BE}/U_T} - 1 \right) \approx I_{ES} e^{v_{BE}/U_T} \quad \text{if F.B.}$$

$$U_T = \text{Thermal voltage} = \frac{kT}{q} = 25.9 \text{ mV} \quad \text{at } T = 300 \text{ K}$$

$I_{ES}$  = saturation current

Simple current mirror

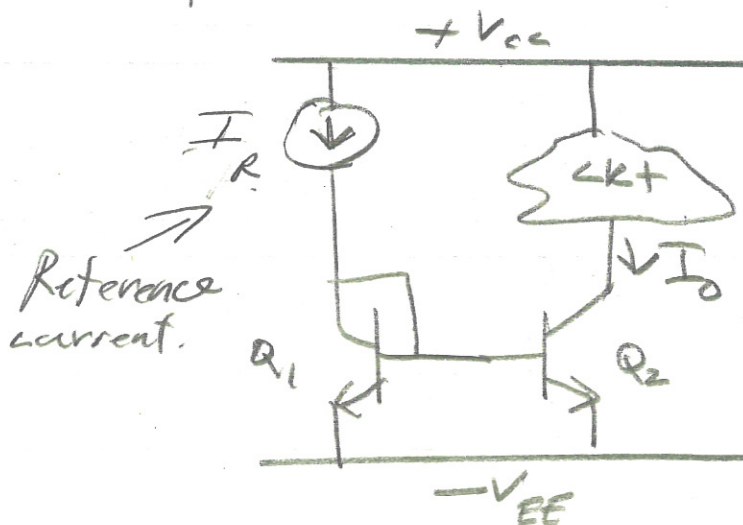


Output current

$$I_O = I_R \quad \text{if}$$

$\beta = \infty, V_A = \infty$   
and  $Q_1, Q_2$  matched!

$$I_{ES1} = I_{ES2}$$

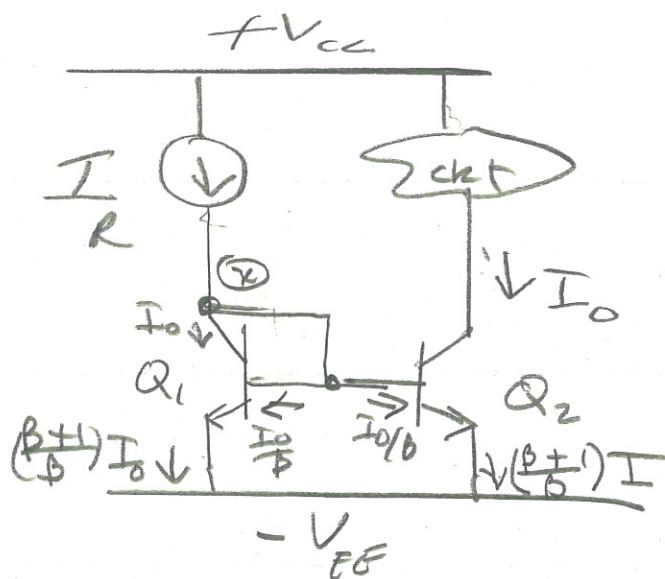

$\beta$  is finite  
 $V_A = \infty$   
 $V_{CE2} > V_{CE,SAT}$   
 $Q_1, Q_2$  matched

$I_{E1} = I_{E2}$  since  $V_{BE1} = V_{BE2}$  and the transistors are matched ( $I_{ES1} = I_{ES2}$ )!

Write KCL at node (x)


$$I_R = \frac{I_0}{\beta} + \frac{I_0}{\beta} + I_0 = I_0 \left(1 + \frac{2}{\beta}\right)$$

So  $\boxed{I_0 = \frac{I_R}{(1 + \frac{2}{\beta})}}$

Note as  $\beta \rightarrow \infty$ ,  
 $I_0 \rightarrow I_R$ !

$I_0 \approx I_R \left(1 - \frac{2}{\beta}\right)$  Taylor Expansion!

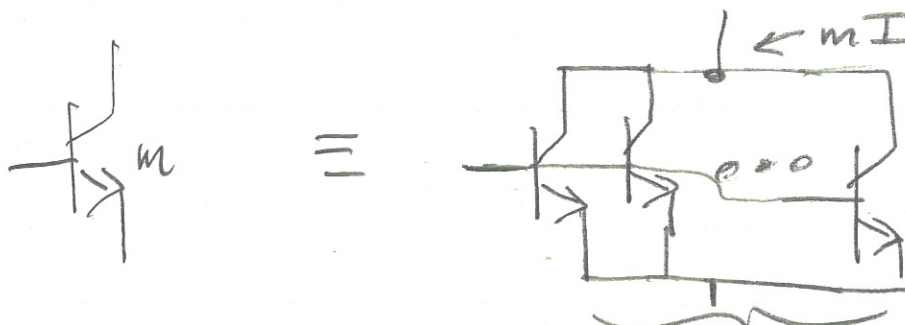
If  $\beta = 100$  the  $I_0$  is  $\sim 2\%$  less than  $I_R$ !



Each BJT carries current  $I$  so total current is  $mI$  says KCL!

$m$  BJTs in parallel


3

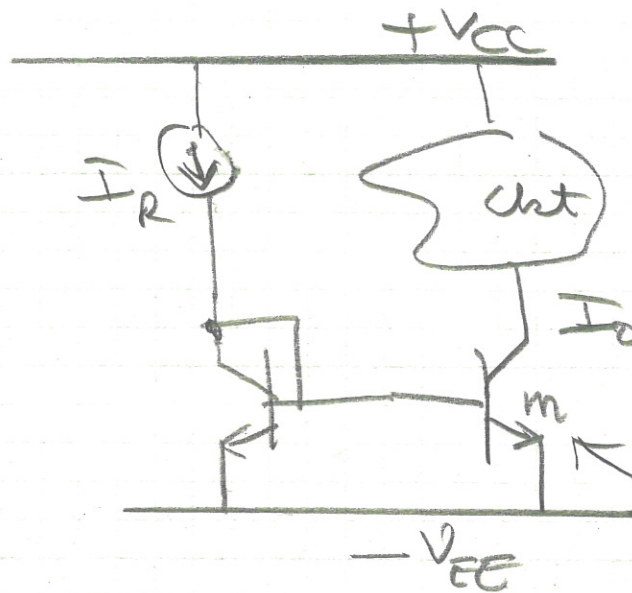

$\beta = \infty$   
 $V_A = \infty$   
 BJTs matched

multiplier,  $m$   
 $m$  BJTs in parallel so  
 $m$  times the current.

How do you build,  $I_R$ ?

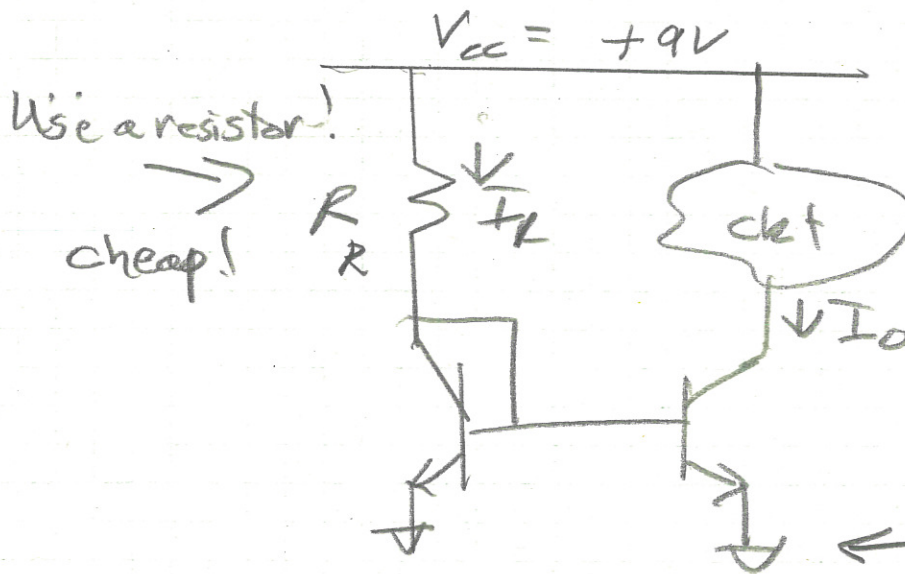

$$I_R = \frac{V_{CC} - V_{BE}}{R_R} = \frac{9V - 0.7}{R_R}$$


If  $R_R = 1k\Omega$ , then  $I_R = 8.3mA$

$$R_R = \frac{V_{CC} - V_{BE(on)}}{I_R}$$

If  $V_{CC}$  changes then  $I_R$  changes. (4)

We have a current source that is sensitive to supply voltage.

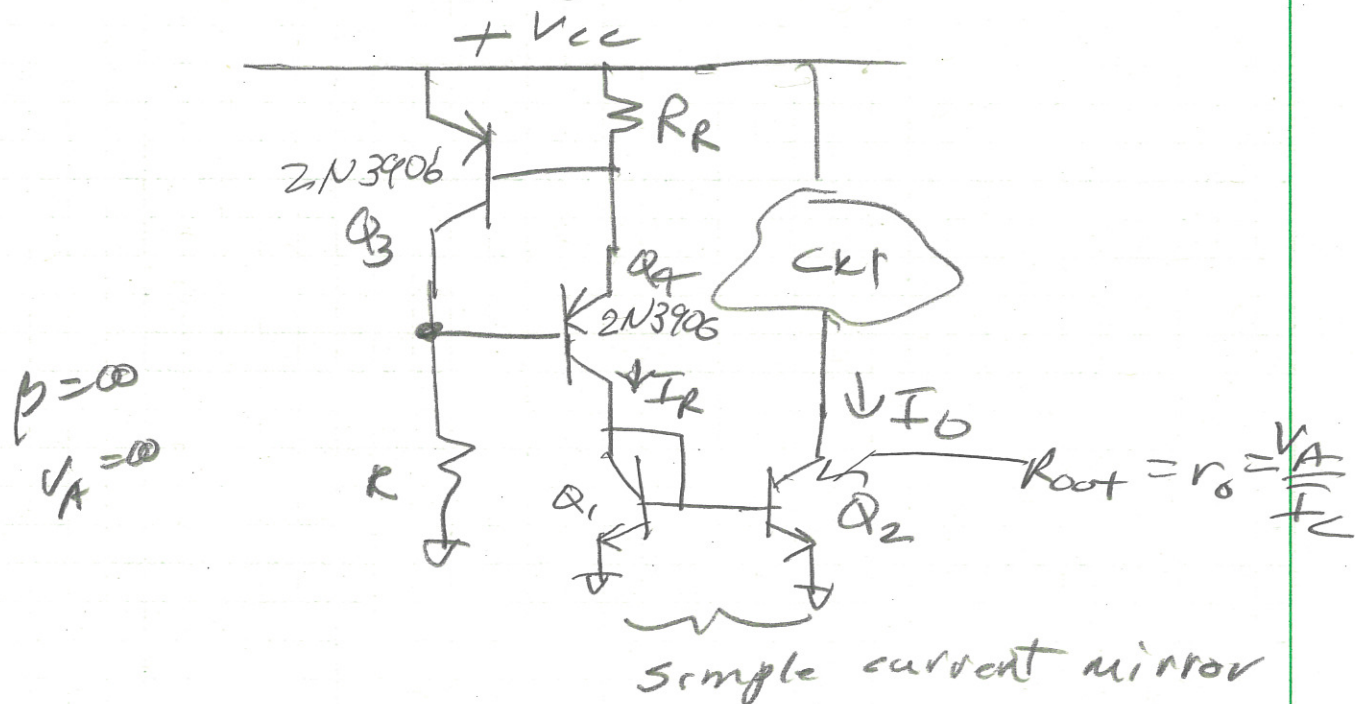Here is how to build a current source less sensitive to supply voltage.



$Q_1, Q_2$  perhaps 2N3904s

$R$  just turns  $Q_3$  on so that  $V_{EB} \approx 0.7$

$$\left| \frac{I_R}{R_R} = \frac{V_{EB}}{R_R} \right| \Rightarrow \left| R_R = \frac{V_{EB}}{I_R} \right|$$

If  $R_R = 1K$  then  $I_R = \frac{0.7V}{1K} = 700\mu A$ .

Value of  $R$  not critical.


When in doubt use  $10K$ .

So make  $R = 10K\Omega$ .

# Section 8.6.2

(5)

## Widlar Current Mirror

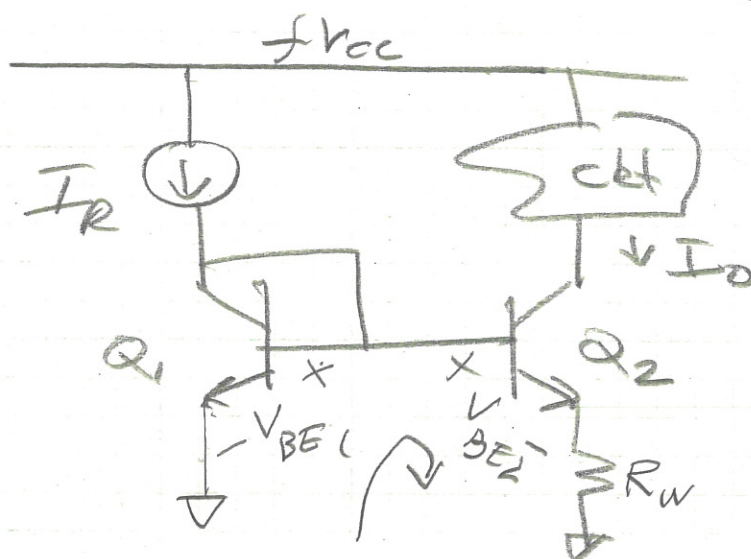

$\beta = \infty$   
 $V_A = \infty$   
 Matched BJTs

KVL

$$V_{BE1} - V_{BE2} - I_O R_W = 0 \quad (1)$$

Recall  $I_E \approx I_{ES} e^{V_{BE}/V_T} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_E}{I_{ES}}\right)$

So eqn (1) becomes

$$V_T \ln\left(\frac{I_R}{I_{ES}}\right) - V_T \ln\left(\frac{I_O}{I_{ES}}\right) - I_O R_W = 0$$

Recall  $\ln(a/b) = \ln(a) - \ln(b)$

$$V_T \ln\left(\frac{I_R}{I_O}\right) = I_O R_W$$

$$R_W = \frac{V_T \ln\left(\frac{I_R}{I_O}\right)}{I_O} *$$


6

Suppose we have a reference current of  $1\text{mA}$  and we want an output current of  $100\mu\text{A}$ , what  $R_W$  should we use.

$$R_W = \frac{V_T \ln\left(\frac{1\text{mA}}{100\mu\text{A}}\right)}{0.1\text{mA}} \approx \frac{60\text{mV}}{0.1\text{mA}}$$


$$R_W = 0.6\text{k}\Omega = 600\Omega!$$


We can also do current multiplication

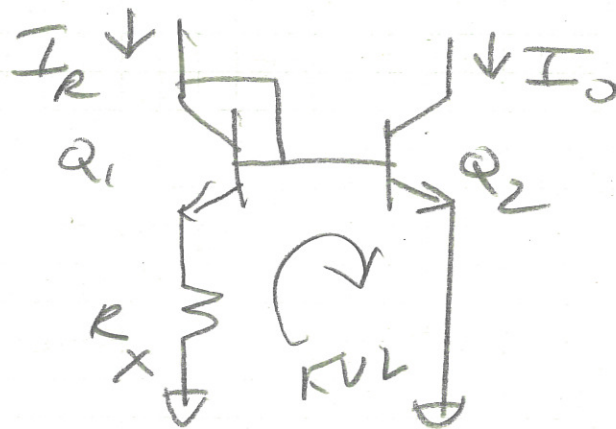

Can relate  $I_O$  to  $I_R$  by writing KVL around the loop!

Darlington pair section 8.7.2

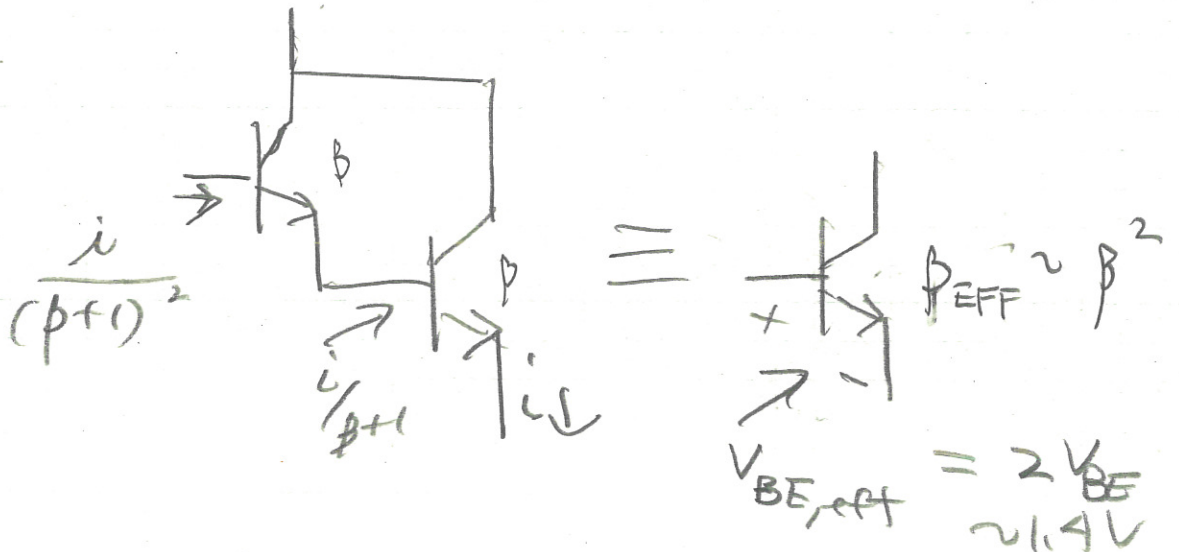

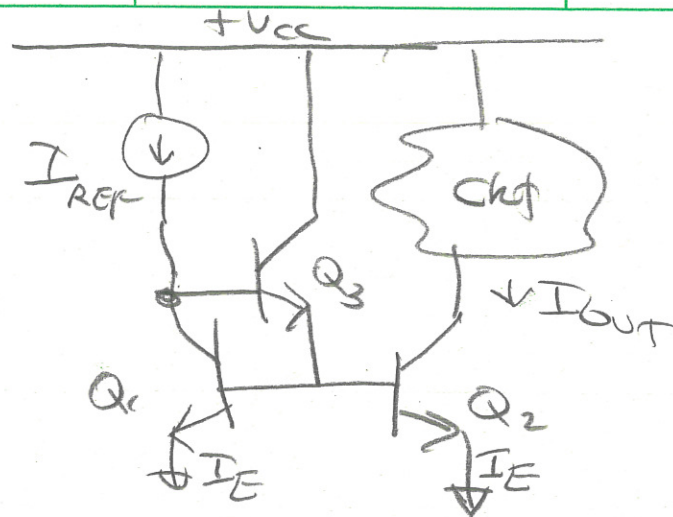

$$I_{E3} = \frac{2 I_E}{\beta + 1} = \frac{2}{\beta} \left( \frac{\beta}{\beta + 1} I_E \right) \leftarrow I_{OUT}$$

$$I_{OUT} = \left( \frac{\beta}{\beta + 1} \right) I_E = I_C \Rightarrow I_C = \frac{\beta + 1}{\beta} I_{OUT}$$

$$I_{REF} = I_C + \frac{I_{E3}}{\beta + 1}$$

$$I_{REF} = \frac{\beta + 1}{\beta} I_{OUT} + \frac{2 I_{OUT}}{\beta (\beta + 1)}$$

$$I_{REF} = \left[ \frac{(\beta + 1)^2}{\beta (\beta + 1)} + \frac{2}{\beta (\beta + 1)} \right] I_{OUT}$$


$$I_{OUT} = \left[ \frac{\beta (\beta + 1)}{(\beta + 1)^2 + 2} \right] I_{REF}$$

$$\approx \frac{1}{1 + \frac{2}{\beta^2}}$$

Base current compensation

Find output resistance of N. lar current mirror

②

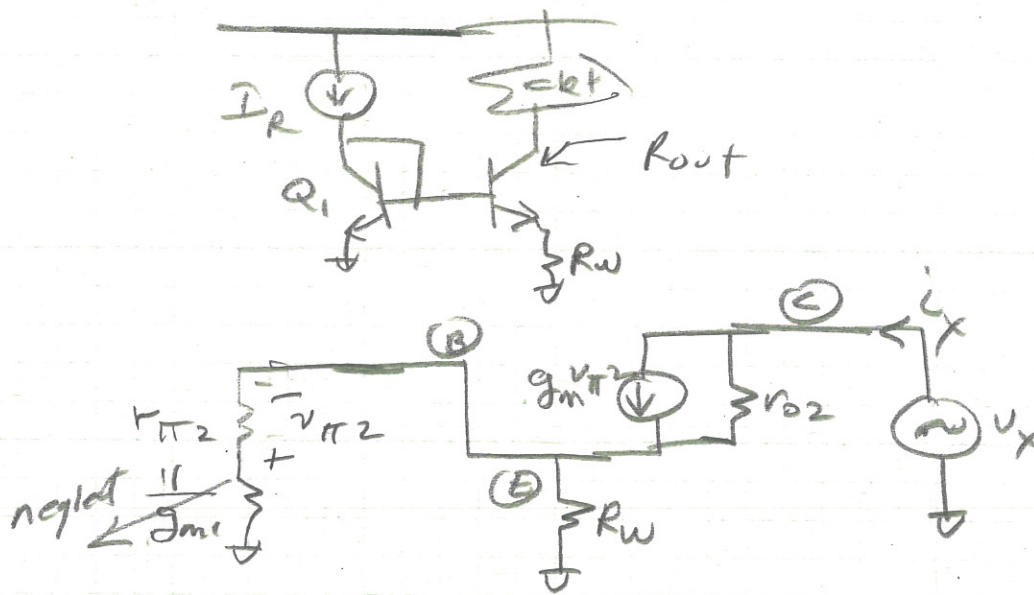

Write KCL at (C) node

$$i_x = g_{m2} v_{\pi 2} + (v_x - v_e) g_{o2}$$

$$\text{But } v_{\pi 2} \approx -v_e$$

$$i_x = -g_{m2} v_e - v_e g_{o2} + v_x g_{o2}$$

$$\text{But } v_e = i_x (R_W \parallel r_{\pi 2}) = i_x \left( \frac{1}{g_w + g_{\pi 2}} \right)$$

$$i_x = -(g_{m2} + g_{o2}) i_x \left( \frac{1}{g_w + g_{\pi 2}} \right) + v_x g_{o2}$$

$$i_x \left[ 1 + \frac{g_{m2} + g_{o2}}{g_w + g_{\pi 2}} \right] = v_x g_{o2}$$

$$R_{out} = \frac{v_x}{i_x} = r_{o2} \left[ 1 + \frac{g_{m2} + g_{o2}}{g_w + g_{\pi 2}} \right]$$

$$\text{If } g_{\pi 2} \ll g_w \text{ \& } g_{o2} \ll g_{m2}$$

$$R_{out} \approx r_{o2} [1 + g_{m2} R_W]$$