

ECE 476 Spring 2021
Chapter 9 Homework

Dr. George Engel

Due one week after we finish chapter

Problem 1. Section 9.2 - BJT Differential Amplifier

Textbook problem 9.27

Problem 2. Section 9.2 - BJT Differential Amplifier

Textbook problem 9.38

Problem 3. Section 9.2 - BJT Differential Amplifier

Textbook problem 9.52

Problem 4. Section 9.3 - Common Mode Rejection

Textbook problem 9.61