

ECE 584
Chapter 1 Homework

Dr. George Engel

Due: One week after we finish covering relevant material.

You should use the $0.35\ \mu\text{m}$ process data given to you in class to answer the following questions. Assume V_{DD} is 3.3 Volts.

Problem 1. Resistor Implementation

Assume matching is important. By design I mean determine both the width and the length of the resistor.

- (a) Design a $8.2K\ K\Omega$ RPOLYH unit resistor.
- (b) Design a $0.65\ K\Omega$ RPOLY2 unit resistor.
- (c) Design a $15.0\ K\Omega$ unit resistor with a zero tempco.

Problem 2. Capacitor Implementation

Assume matching is important. By design, I mean determine both the width and the length of the capacitor.

- (a) Design a $0.8\ \text{pF}$ double-poly unit capacitor.
- (b) Design a $2.5\ \text{pF}$ double-poly unit capacitor.

Problem 3. Transistor Used as a Resistor

- (a) Design a $100\ \text{k}\Omega$ resistor by using a NMOS device. Assume the source voltage is 1.65 Volts and the gate is tied to V_{DD} . For what range of V_{DS} voltage will the "resistor" be reasonably linear?
- (b) Design a $100\ \text{k}\Omega$ resistor by using a PMOS device. Assume the source voltage is 1.65 Volts and the gate is tied to **GND**. For what range of V_{DS} voltage will the "resistor" be reasonably linear?

Problem 4. Inversion Coefficient

Assume a NMOS transistor length of $2\ \mu\text{m}$ in this problem and a quiescent drain-source current of $10\ \mu\text{A}$.

- (a) Determine the width of the NMOS transistor so that the inversion coefficient, θ , is 0.05 *i.e.* weakly inverted.
- (b) Determine the width of the NMOS transistor so that the inversion coefficient, θ , is 3 *i.e.* moderately inverted.
- (c) Determine the width of the NMOS transistor so that the inversion coefficient, θ , is 100 *i.e.* strongly inverted.

Problem 5. Small-Signal Transconductance

Assume a NMOS transistor length of $2 \mu m$ in this problem and a quiescent drain-source current of $8 \mu A$.

- (a) Determine the small-signal transconductance when θ is 0.05.
- (b) Determine the small-signal transconductance when θ is 3.
- (c) Determine the small-signal transconductance when θ is 100.

Problem 6. Small-Signal Output Resistance

Assume a NMOS transistor length of $4 \mu m$ in this problem and a quiescent drain-source current of $10 \mu A$.

- (a) Determine the output resistance.
- (b) Determine the saturation or *effective* voltage when θ is 30.
- (c) Determine the saturation or *effective* voltage when θ is 3.