


ECE 584
Chapter 3 Homework

Dr. George Engel

Due: Complete before Midterm Exam

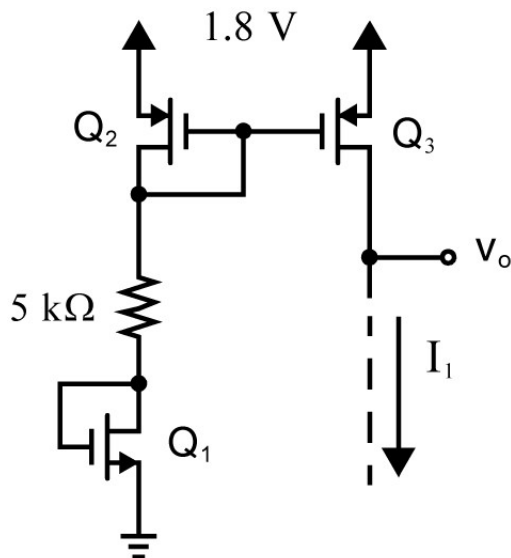Problem 1. (Current Source Design)

Consider the current source shown below. FETs Q_2 and Q_3 are matched. Rather than the 1.8 Volt supply pictured, assume $V_{DD} = 3.3$ Volts.




- Determine the shape factor of Q_1 so that V_{GS} is 1.0 Volts.
- Determine the shape factor of Q_2 and Q_3 so that V_{SG} for these devices is 1.0 Volts.
- What is the DC output current, I_1 ?
- Size all transistors so that the output resistance of the current source is at least $500\text{ k}\Omega$.
- What is the compliance of the mirror?
- Clearly indicate the size (W , L , and m values) for all FETS on the Figure.

Problem 2. (Cascode Current Source Mirror)


Consider the cascode current source shown in the figure below. Assume that transistors Q_1 and Q_2 are matched. Also, assume that transistors Q_3 and Q_4 are matched. Please neglect any body effects.

- Draw a small-signal equivalent circuit.
- Derive an expression for the small-signal output resistance of the circuit. Make any reasonable approximations so as to simplify the resulting expression.
- What is the output compliance of the mirror?

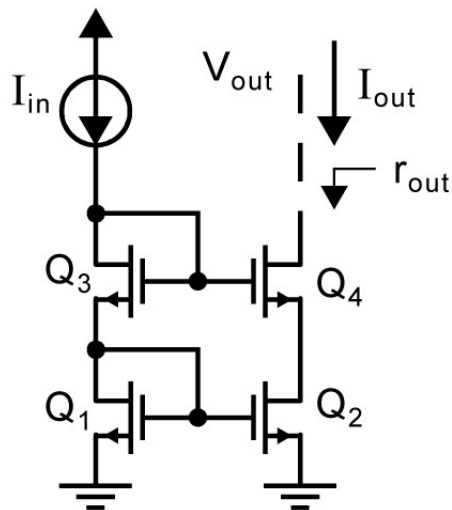

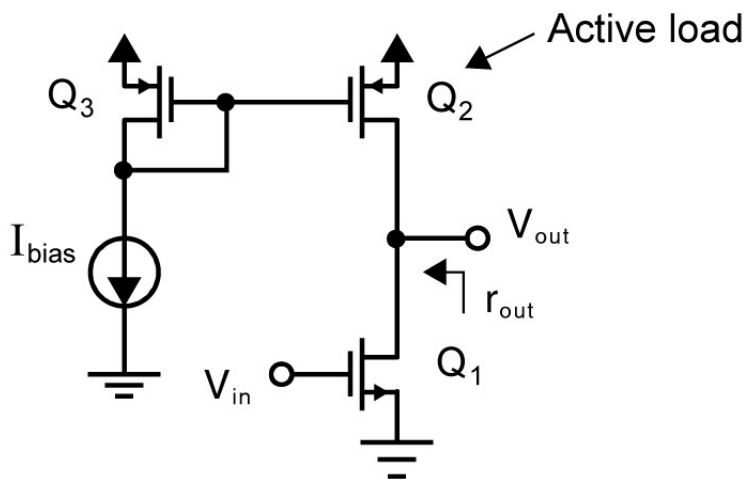Problem 3. (Design of a Common Source Amplifier)


Consider the common source amplifier with active load pictured below. Assume $V_{DD} = 3.3\text{ V}$ and that I_{bias} is $15\ \mu\text{A}$. Moreover, assume Q_2 and Q_3 are matched. The length of all devices is $3\ \mu\text{m}$.



- Choose $\theta_1 = 3$ and compute the transconductance of transistor, Q_1 .
- What is the saturation *i.e.* the effective voltage of transistor, Q_1 ?
- Determine the shape factor of Q_2 so that the effective voltage of the device is 400 mV.
- Determine the output resistance of the amplifier?
- What is the low-frequency gain of this CS amplifier?
- What is the amplifier's maximum voltage swing?
- Clearly indicate the size (W, L, and m values) for all FETS on the Figure.

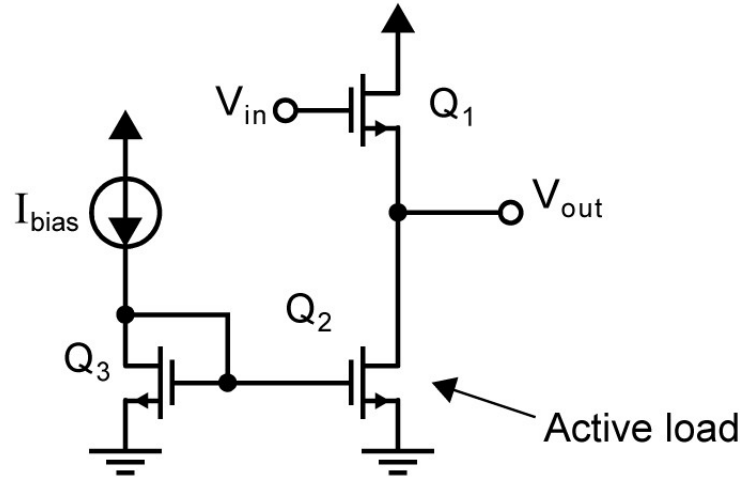Problem 4. (Design of a Source Follower)

Consider the source follower pictured below. Assume $V_{DD} = 3.3\text{ V}$ and that I_{bias} is $15\ \mu\text{A}$. Moreover, assume Q_2 and Q_3 are matched. The length of all devices is $3\ \mu\text{m}$. The NFET, Q_1 does suffer from the body effect since the source of the device will be at ground potential.




- Choose $\theta_1 = 3$ and compute the transconductance of transistor, Q_1 .
- What is the saturation *i.e.* effective voltage of transistor, Q_1 ?
- Determine the shape factor of Q_2 so that the saturation voltage of the device is 400 mV.
- Determine the output resistance of the amplifier?
- What is the low-frequency gain of this source-follower circuit?
- What is the amplifier's maximum voltage swing?
- Clearly indicate the size (W, L, and m values) for all FETS on the Figure.

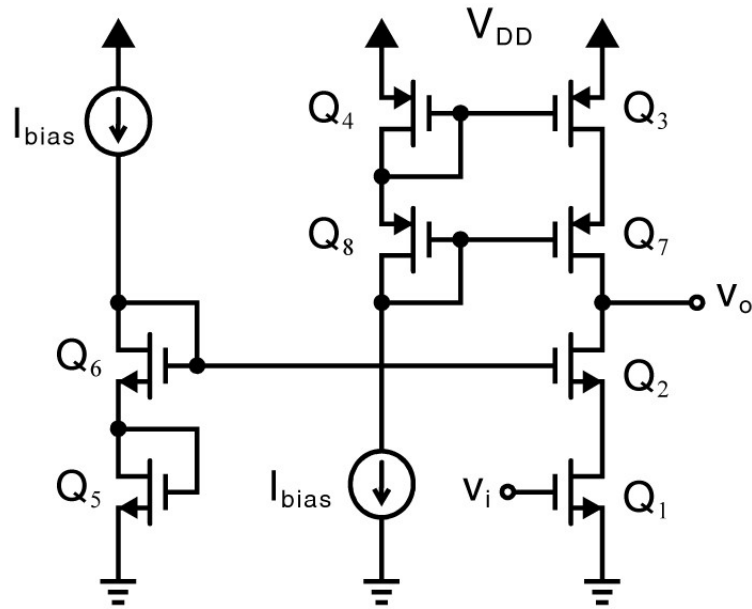Problem 5. (Single-Ended Cascode Amplifier)

Consider the cascode amplifier depicted on the following page. Assume $V_{DD} = 3.3\text{ V}$ and that I_{bias} is $15\ \mu\text{A}$. Transistors Q_3, Q_4 are matched as well as Q_7 , and Q_8 . Moreover, assume transistors Q_2, Q_5 and Q_6 are matched. The length of all devices is $3\ \mu\text{m}$.

- Choose $\theta_1 = 3$ and compute the transconductance of transistor, Q_1 .
- What is the saturation *i.e.* effective voltage of transistor, Q_1 ?
- Determine the shape factor of Q_2 so that the saturation voltage of the device is 250 mV.



- (d) Determine the shape factor of Q_3 so that the saturation voltage of the device is 250 mV.
- (e) Determine the shape factor of Q_7 so that the saturation voltage of the device is 250 mV.
- (f) Determine the output resistance of the amplifier?
- (g) What is the low-frequency gain of the cascode amplifier?
- (h) What is the amplifier's maximum voltage swing?
- (i) Clearly indicate the size (W , L , and m values) for all FETS on the Figure.