

4.10. Limiters

- ✧ **Limiter** is a nonlinear circuit with an output saturation characteristic
- ✧ It rejects envelope variations but preserves the phase variations.

$$v_{in}(t) = R(t) \cos[w_c t + \theta(t)]$$



$$v_{out}(t) = KV_L \cos[w_c t + \theta(t)]$$


Where K is the level of the fundamental component of the square wave, $4/\pi$, multiplied by the gain of the output (bandpass) filter. V_L is output limits.

4.11. Mixers, Up Converters, Down Converters

➤ **Ideal mixer** is a mathematical multiplier of two input signals. One of the signals is sinusoidal generated by a local oscillator. Mixing results in frequency translation.

➤ Mixers are used to obtain frequency translation of the input signal.

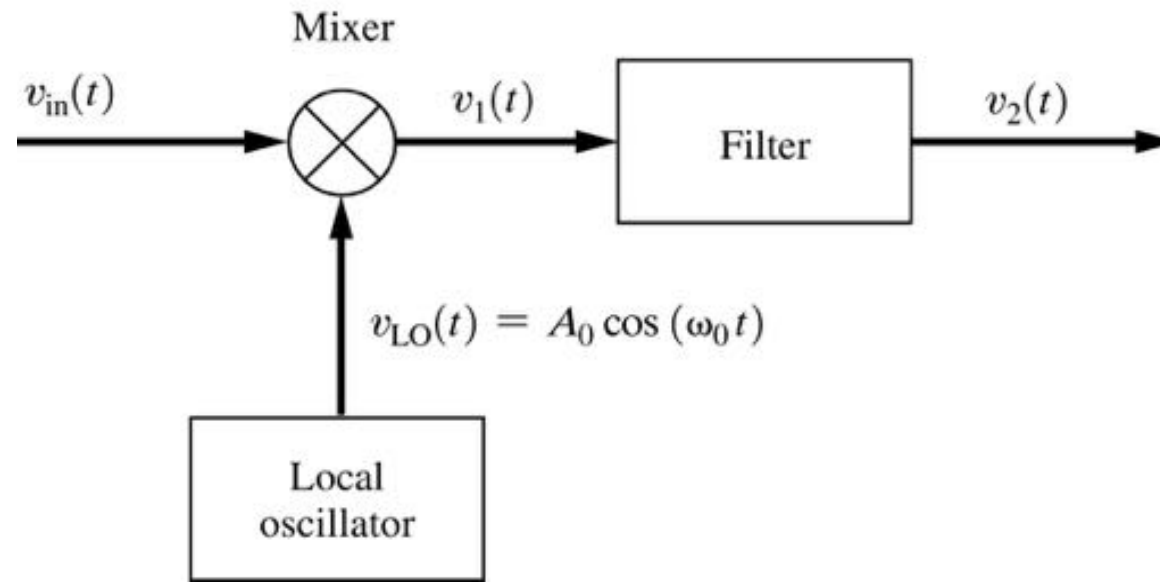where $V_{in}(t)$ is bandpass signal: $v_{in}(t) = \text{Re} \left\{ g_{in}(t) e^{j\omega_c t} \right\}$



4.11. Mixers, Up Converters, Down Converters

Bandpass Input Signal

$$v_{in}(t) = \text{Re}\{g_{in}(t)e^{j\omega_c t}\}$$

Mixer Output

$$\begin{aligned}v_1(t) &= \left[A_0 \text{Re}\{g_{in}(t)e^{j\omega_c t}\} \right] \cos \omega_0 t \\&= \frac{A_0}{4} \left[g_{in}(t)e^{j\omega_c t} + g_{in}^*(t)e^{-j\omega_c t} \right] (e^{j\omega_0 t} + e^{-j\omega_0 t}) \\&= \frac{A_0}{4} \left[g_{in}(t)e^{j(\omega_c + \omega_0)t} + g_{in}^*(t)e^{-j(\omega_c + \omega_0)t} + g_{in}(t)e^{j(\omega_c - \omega_0)t} + g_{in}^*(t)e^{-j(\omega_c - \omega_0)t} \right]\end{aligned}$$

$$\text{Re}\{\cdot\} = \frac{1}{2}\{\cdot\} + \frac{1}{2}\{\cdot\}^*$$

$$v_1(t) = \frac{A_0}{2} \text{Re}\{g_{in}(t)e^{j(\omega_c + \omega_0)t}\} + \frac{A_0}{2} \text{Re}\{g_{in}(t)e^{j(\omega_c - \omega_0)t}\}$$

$$f_u = f_c + f_0$$

$$f_d = f_c - f_0$$

UPCONVERSION

DOWNCONVERSION

BANDPASS FILTER

BASEBAND OR BANDPASS FILTER

4.11. Mixers, Up Converters, Down Converters

$$v_1(t) = \frac{A_0}{2} \operatorname{Re} \left\{ \underbrace{g_{in}(t) e^{j(\omega_c + \omega_0)t}}_{\text{Up-conversion}} \right\} + \frac{A_0}{2} \operatorname{Re} \left\{ \underbrace{g_{in}(t) e^{j(\omega_c - \omega_0)t}}_{\text{Down-conversion}} \right\}$$

$$f_u = f_c + f_0$$

$$f_d = f_c - f_0$$



Bandpass Filter



Baseband/bandpass
Filter ($f_c - f_0$)

4.11. Mixers, Up Converters, Down Converters

- If $(f_c - f_0) = 0$ → Low Pass Filter gives baseband spectrum
- If $(f_c - f_0) > 0$ → Bandpass filter → Modulation is preserved

Filter Output:
$$v_2(t) = \text{Re}\{g_2(t)e^{j(\omega_c - \omega_0)t}\} = \frac{A_0}{2} \text{Re}\{g_{in}(t)e^{j(\omega_c - \omega_0)t}\}$$

- If $f_c > f_0$ → modulation on the mixer input is preserved

- If $f_c < f_0$ →
$$v_1(t) = \frac{A_0}{2} \text{Re}\{g_{in}(t)e^{j(\omega_c + \omega_0)t}\} + \frac{A_0}{2} \text{Re}\{g_{in}^*(t)e^{j(\omega_0 - \omega_c)t}\}$$

' ω ' needs to be positive

4.11. Mixers, Up Converters, Down Converters

- Complex envelope of an **Up Converter**:

$$g_2(t) = \frac{A_0}{2} g_{in}(t); \quad f_u = f_c + f_0 > 0 \quad - \text{Amplitude is scaled by } A_0/2$$

- Complex envelope of a **Down Converter**:

$$f_d = f_c - f_0 > 0 \quad \text{i.e., } f_0 < f_c \rightarrow \text{down conversion with } \textit{low-side injection}$$

$$g_2(t) = \frac{A_0}{2} g_{in}(t) \quad - \text{Amplitude is scaled by } A_0/2$$


$$f_d = f_0 - f_c > 0 \quad \text{i.e., } f_0 > f_c \rightarrow \text{down conversion with } \textit{high-side injection}$$

$$g_2 = \frac{A_0}{2} g_{in}^*(t) \quad - \text{Amplitude is scaled by } A_0/2$$

- Sidebands are reversed from those on the input

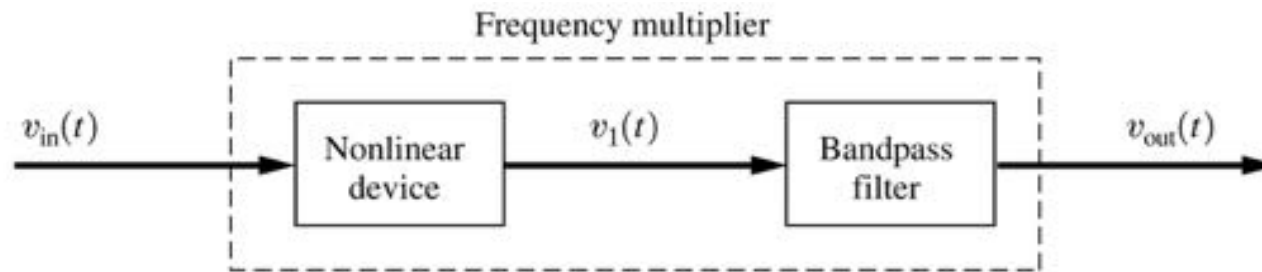4.12. Frequency Multipliers

➤ **Frequency Multipliers** consists of a nonlinear device together with a tuned circuit. The frequency of the output is n times the frequency of the input.



(a) Block Diagram of a Frequency Multiplier

$$v_{in}(t) = R(t)\cos(\omega_c t + \theta(t))$$

$$v_1(t) = K_n v^{in}(t)$$


$$= K_n R^n(t)\cos^n(\omega_c t + \theta(t))$$

$$v_1(t) = CR^n(t)\cos(n\omega_c t + n\theta(t)) + \text{other terms}$$

$$v_{out}(t) = CR^n(t)\cos(n\omega_c t + n\theta(t))$$

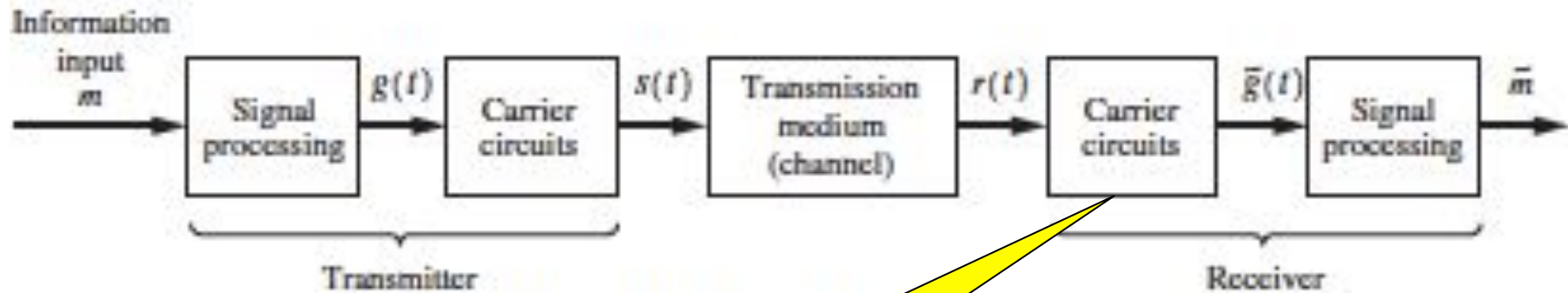4.13. Detector Circuits

➤ **Detectors** convert input bandpass waveform into an output baseband waveform.




Detector Circuits

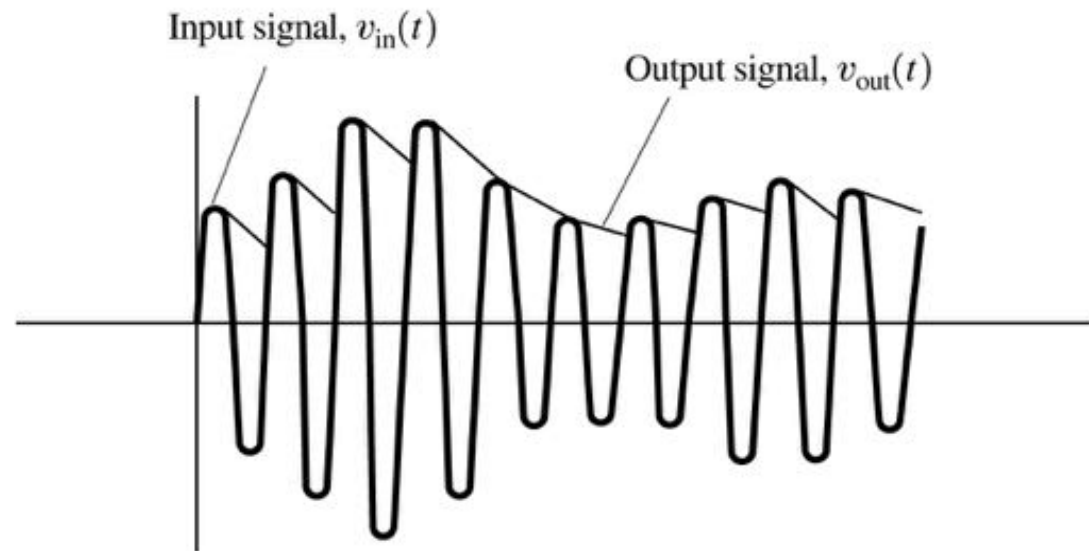4.13. Detector Circuits

Envelope Detector

- **Ideal envelope detector:** Waveform at the output is a real envelope $R(t)$ of its input



Bandpass input: $v_{in}(t) = R(t)\cos[\omega_c t + \theta(t)] \quad R(t) \geq 0$

Envelope Detector Output: $v_{out}(t) = KR(t)$

K – Proportionality Constant

4.13. Detector Circuits

Envelope Detector

The envelope detector is typically used to detect the modulation on AM signal. The detected DC is used for **Automatic Gain Control (AGC)**.

In this case, the complex envelope of the input signal


$$g(t) = A_c[1+m(t)].$$

$$\begin{aligned}v_{out}(t) &= KR(t) \\ &= K|g(t)| \\ &= KA_c[1+m(t)] \\ &= \text{DC} + \text{Message}\end{aligned}$$

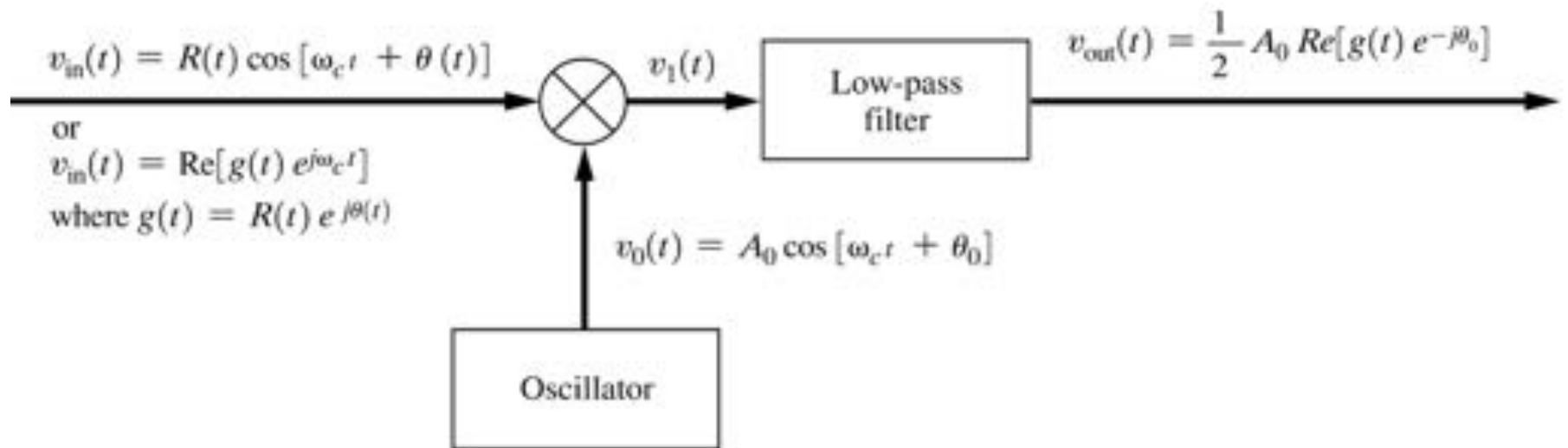4.13. Detector Circuits

Product Detector

Product Detector is a Mixer circuit that down converts input to baseband.



f_c - Freq. of the oscillator

ϑ_0 - Phase of the oscillator

4.13. Detector Circuits

Product Detector

Output of the multiplier:

$$\begin{aligned}v_1(t) &= R(t) \cos[\omega_c t + \theta(t)] A_0 \cos(\omega_c t + \theta_0) \\ &= \frac{1}{2} A_0 R(t) \cos[\theta(t) - \theta_0] + \frac{1}{2} A_0 R(t) \cos[2\omega_c t + \theta(t) + \theta_0]\end{aligned}$$

Low-pass Filter passes down conversion component:

$$v_{out}(t) = \frac{1}{2} A_0 R(t) \cos[\theta(t) - \theta_0] = \frac{1}{2} A_0 \operatorname{Re}\{g(t) e^{-j\theta_0}\}$$

Where $g(t)$ is the complex envelope of the input and $x(t)$ & $y(t)$ are the quadrature components of the input:

$$g(t) = R(t) e^{j\theta(t)} = x(t) + jy(t)$$

4.13. Detector Circuits

Applications of Product Detector

➤ INPHASE DETECTOR :

$$\text{if } \theta_0 = 0 : \quad \Rightarrow v_{out}(t) = \frac{1}{2} A_0 x(t)$$

➤ QUADRATURE PHASE DETECTOR

$$\text{if } \theta_0 = 90 \quad \Rightarrow v_{out} = \frac{1}{2} A_0 y(t)$$

➤ ENVELOPE DETECTOR

$$\text{if } \theta(t) = 0 \quad \Rightarrow v_{out} = \frac{1}{2} A_0 R(t)$$


➤ **PHASE DETECTOR** If an angle modulated signal is present at the input and reference phase $(\vartheta_0) = 90^\circ$

$$\text{if } \theta_0 = 90^\circ \quad v_{in}(t) = A_c \cos [\omega_c t + \theta(t)]$$

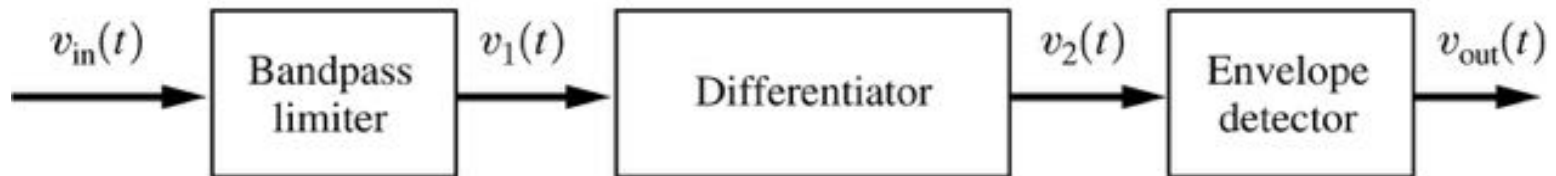4.13. Detector Circuits

Frequency Modulation Detector

➤ **A ideal FM Detector** is a device that produces an output that is proportional to the instantaneous frequency of the input.



4.13. Detector Circuits

Frequency Modulation Detector

Frequency demodulation using slope detection.

$$v_{in}(t) = A(t) \cos[\omega_c t + \theta(t)] \quad \theta(t) = K_f \int_{-\infty}^t m(\tau) d\tau$$

$$v_1(t) = V_L \cos[\omega_c t + \theta(t)] \quad v_2(t) = -V_L \left[\omega_c + \frac{d\theta(t)}{dt} \right] \sin[\omega_c t + \theta(t)]$$

$$v_{out}(t) = \left| -V_L \left[\omega_c + \frac{d\theta(t)}{dt} \right] \right| = V_L \left[\omega_c + \frac{d\theta(t)}{dt} \right] =$$

$$V_L \omega_c + V_L K_f m(t) = \text{DC} + \text{AC (Proportional to } m(t))$$

- The DC output can easily be blocked